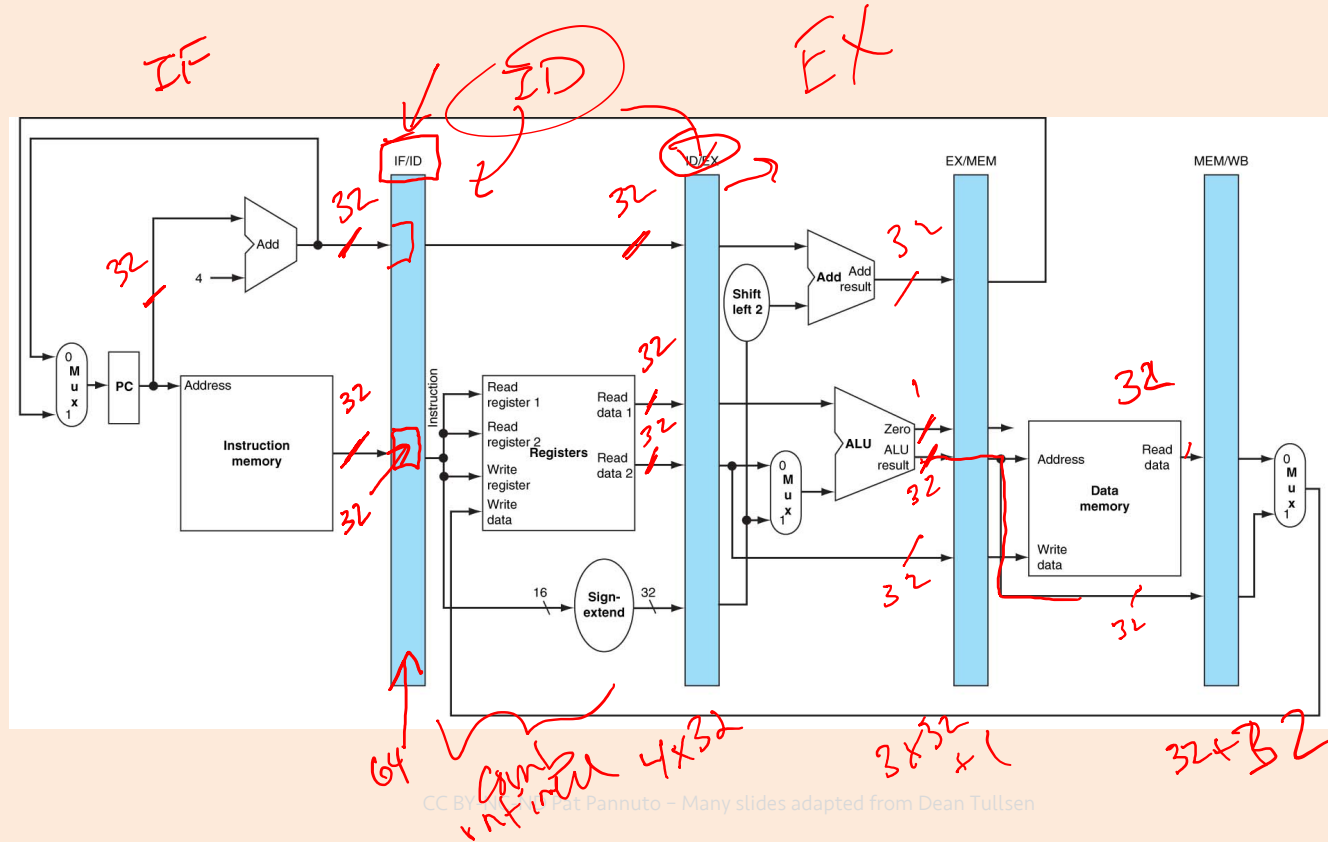


# Poll Q: How many D flip flops are in this pipeline?



# The Pipeline in Execution


**add \$10, \$1, \$2**

Instruction Decode/  
Register Fetch

Execute/  
Address Calculation

Memory Access

Write Back

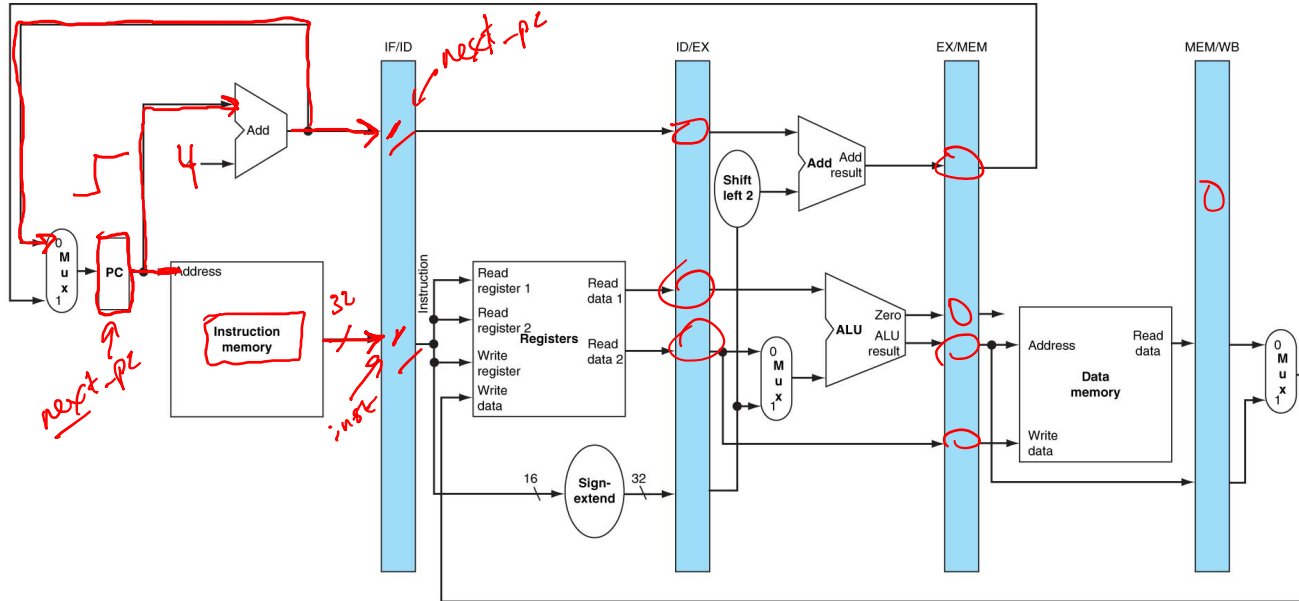

# The Pipeline in Execution


lw \$12, 1000(\$4)

add \$10, \$1, \$2

Execute/  
Address Calculation

Memory Access

Write Back

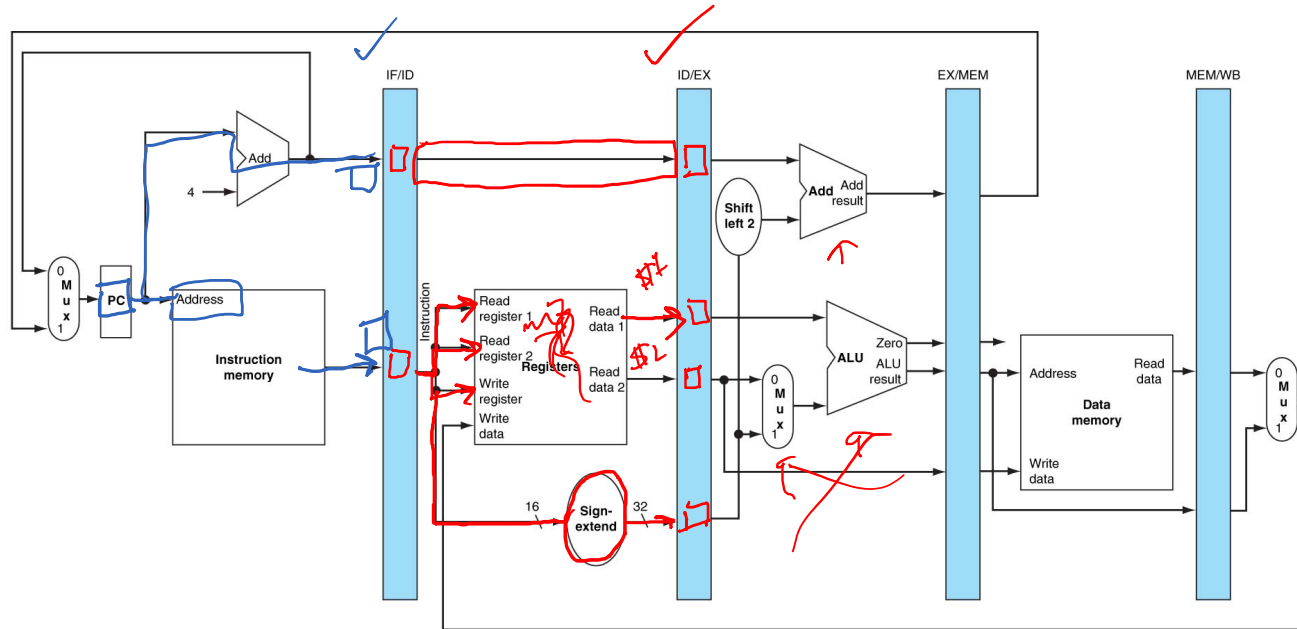


# The Pipeline in Execution

sub \$15, \$4, \$1


*dst*  
*rs1*  
*rs2*  
 lw \$12, 1000(\$4)  
*read reg 2?*

add \$10, \$1, \$2

 


Memory Access

Write Back

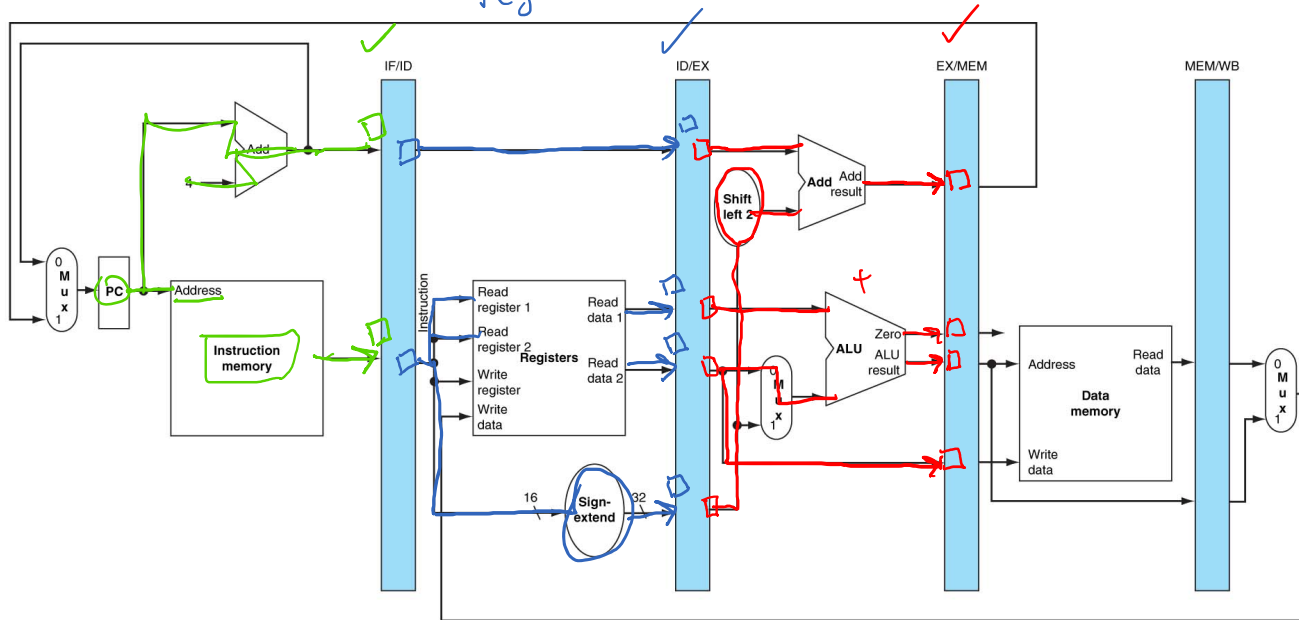

~~Fix flow~~ →

# The Pipeline in Execution

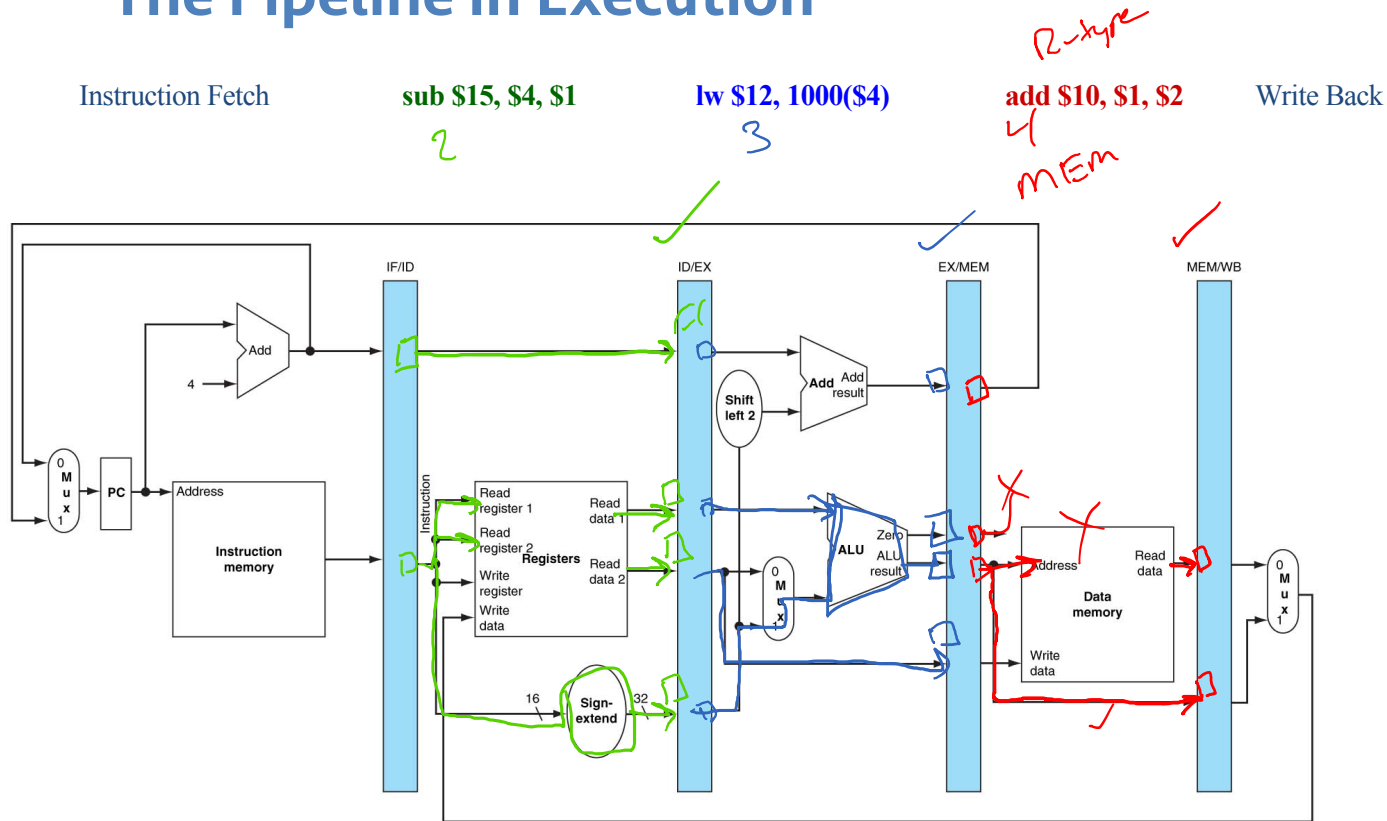

# The Pipeline in Execution


Instruction Fetch

Instruction Decode/  
Register Fetch

**sub \$15, \$4, \$1**

**lw \$12, 1000(\$4)**

**add \$10, \$1, \$2**

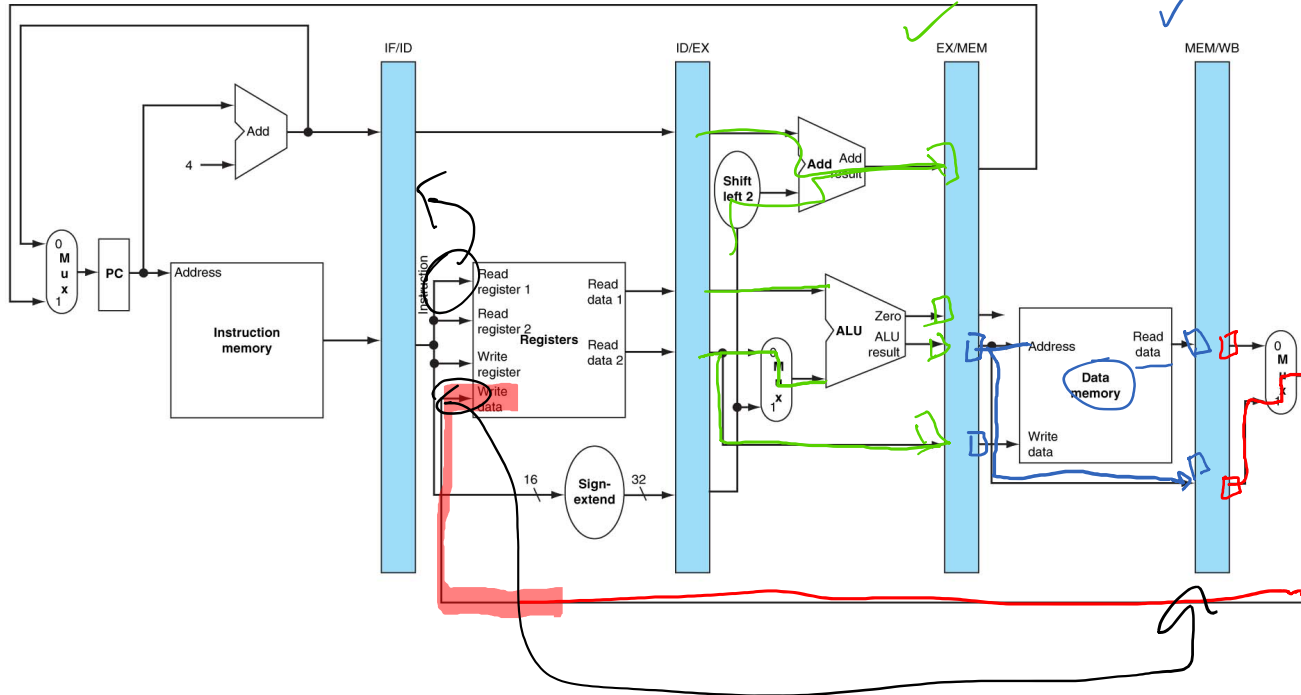

# The Pipeline in Execution

(6th year)


Instruction Fetch

Instruction Decode/  
Register Fetch


Execute/  
Address Calculation

sub \$15, \$4, \$1

lw \$12, 1000(\$4)

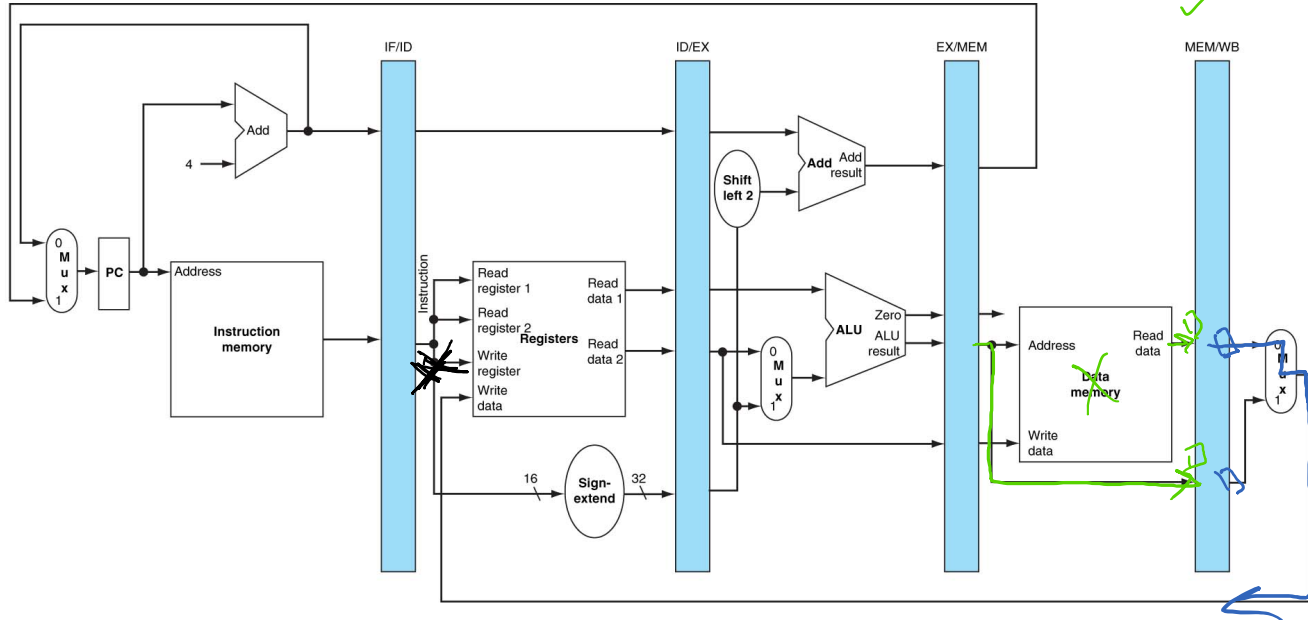

# The Pipeline, with controls But....

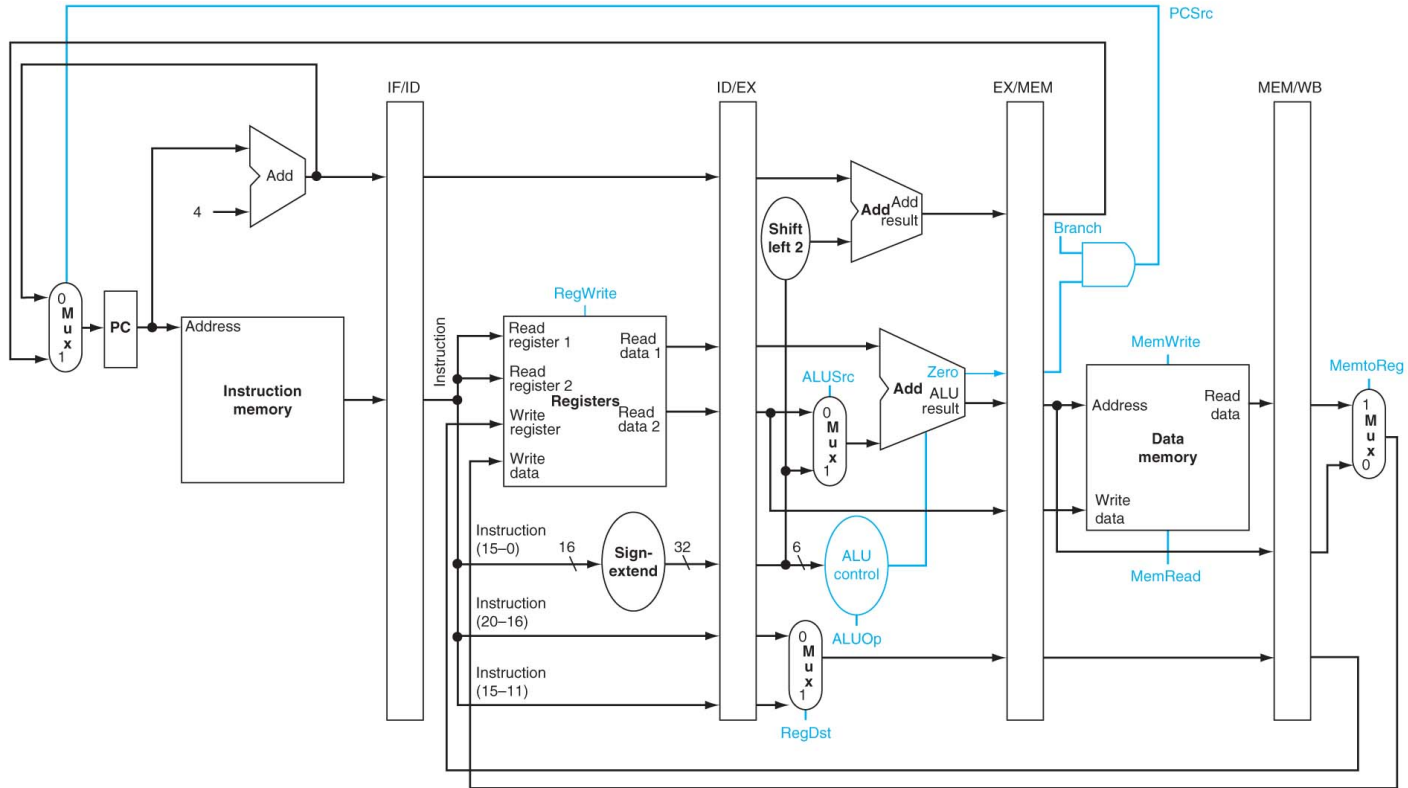



# Pipelined Control

- I told you multicycle control was messy. We would expect pipelined control to be messier.

# Pipelined Control

- I told you multicycle control was messy. We would expect pipelined control to be messier.
  - Why?


# Pipelined Control

- I told you multicycle control was messy. We would expect pipelined control to be messier.
  - Why?
- But it turns out we can do it with just...


# Pipelined Control

- I told you multicycle control was messy. We would expect pipelined control to be messier.
  - Why?
- But it turns out we can do it with just...
- **Combinational logic!**
  - Signals generated **once**
  - Follow instruction through the pipeline

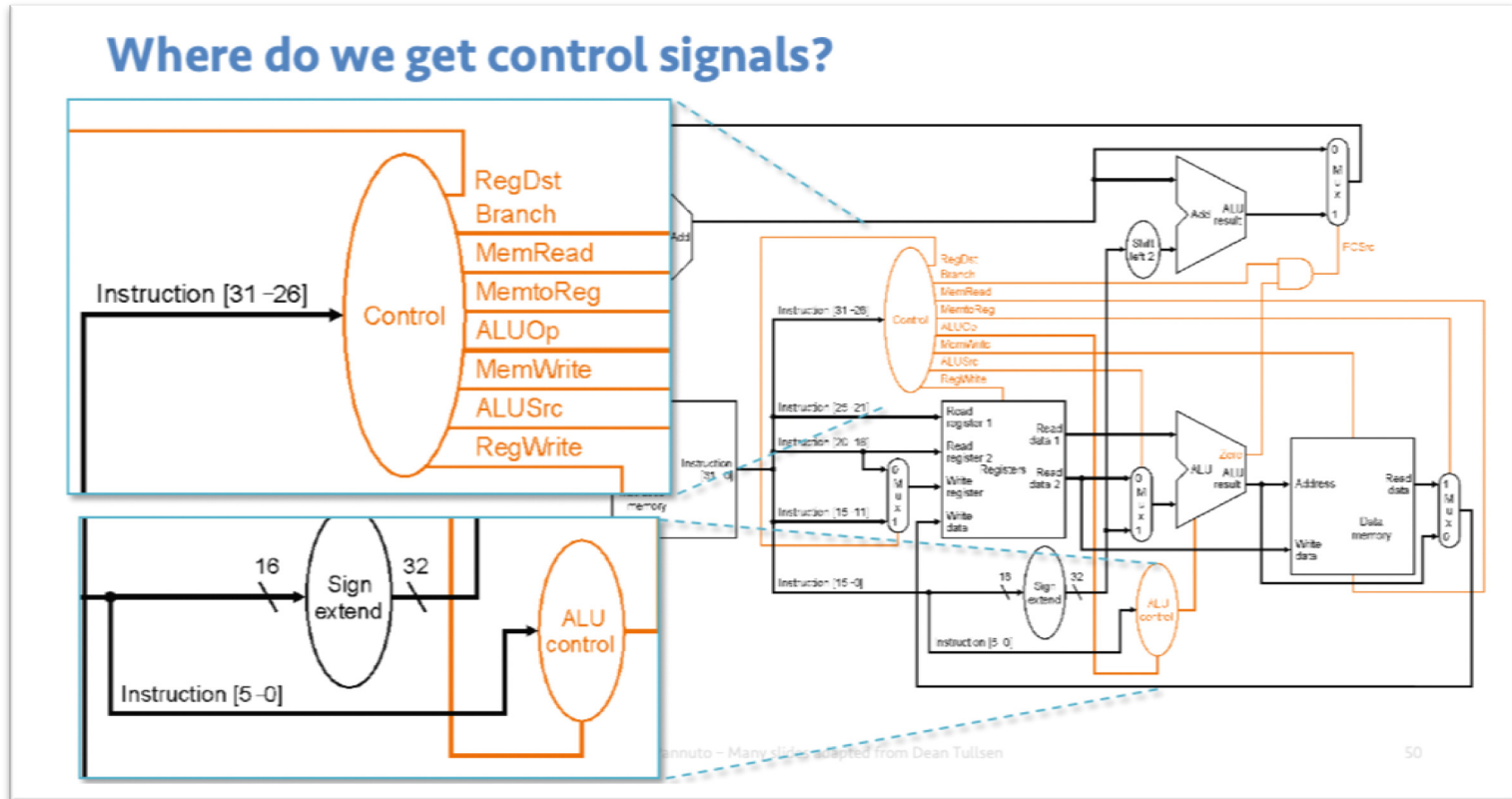
# Recall: Control signals in the single-cycle machine



# Pipelined Control

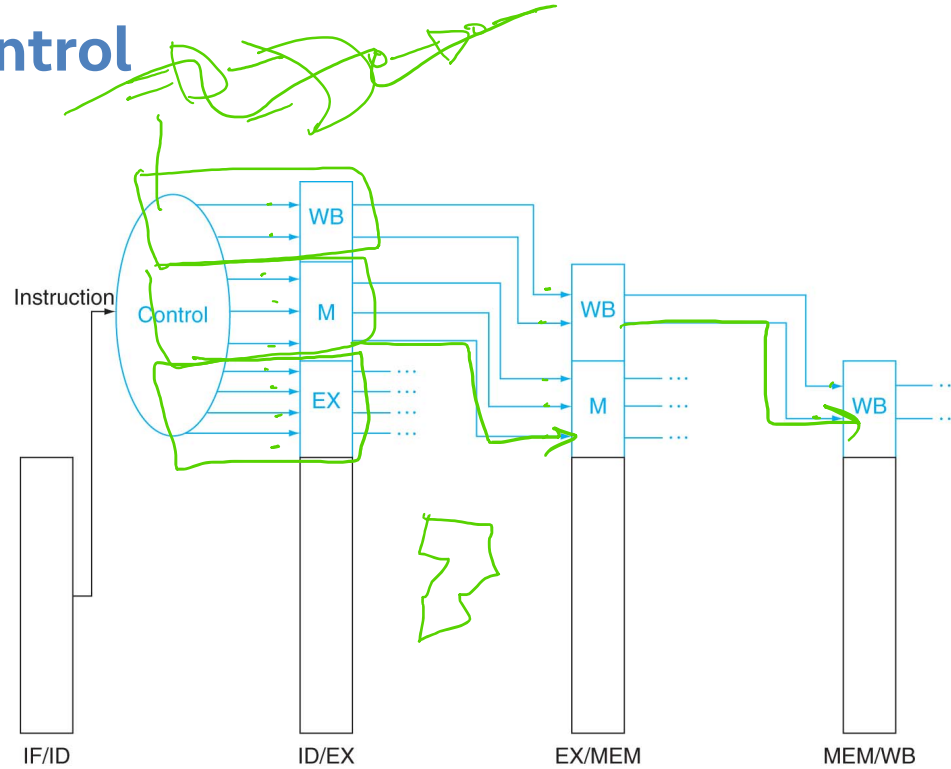


# Pipelined Control

 

So, really it is combinational logic and some registers to propagate the signals to the right stage.

# The Pipeline with Control Logic

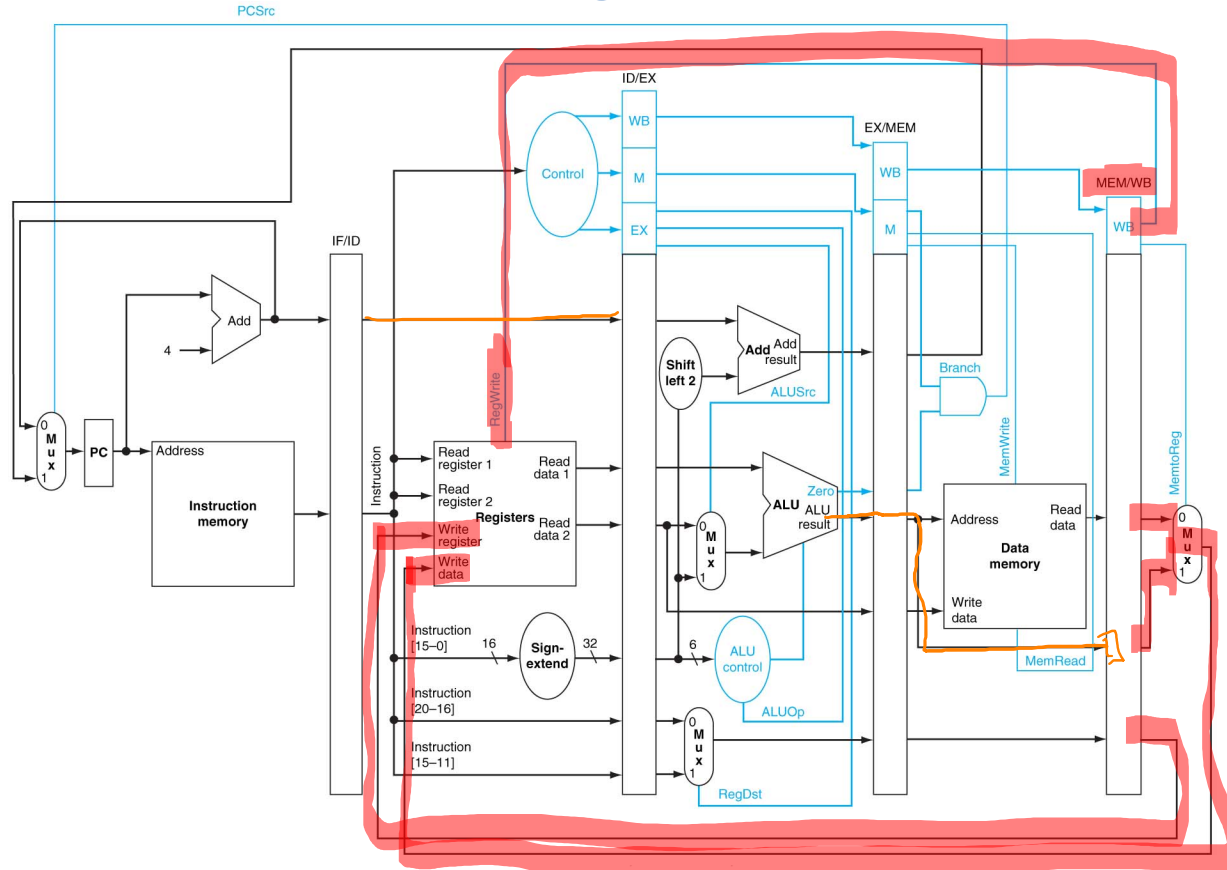




# Pipelined Control Signals

Instruction	Execution Stage Control Lines				Memory Stage Control Lines			Write Back Stage Control Lines	
	RegDst	ALUOp1	ALUOp0	ALUSrc	Branch	MemRead	MemWrite	RegWrite	MemtoReg
R-Format	1	1	0	0	0	0	0	1	0
lw	0	0	0	1	0	1	0	1	1
sw	x	0	0	1	0	0	1	0	x
beq	x	0	1	0	1	0	0	0	x

# Pipelined Control Signals

 

Instruction	Execution Stage Control Lines				Memory Stage Control Lines			Write Back Stage Control Lines	
	RegDst	ALUOp1	ALUOp0	ALUSrc	Branch	MemRead	MemWrite	RegWrite	MemtoReg
R-Format	1	1	0	0	0	0	0	1	0
lw	0	0	0	1	0	1	0	1	1
sw	x	0	0	1	0	0	1	0	x
beq	x	0	1	0	1	0	0	0	x

Let's just do one.

# The Pipeline with Control Logic


Cycle 1

Cycle 2

Cycle 3  
ALUSrc = 5

beq  
RegDst = X  
ALUOp = sub

Cycle 4  
Branch = 1  
MemW =  $\phi$   
MemR =  $\phi$

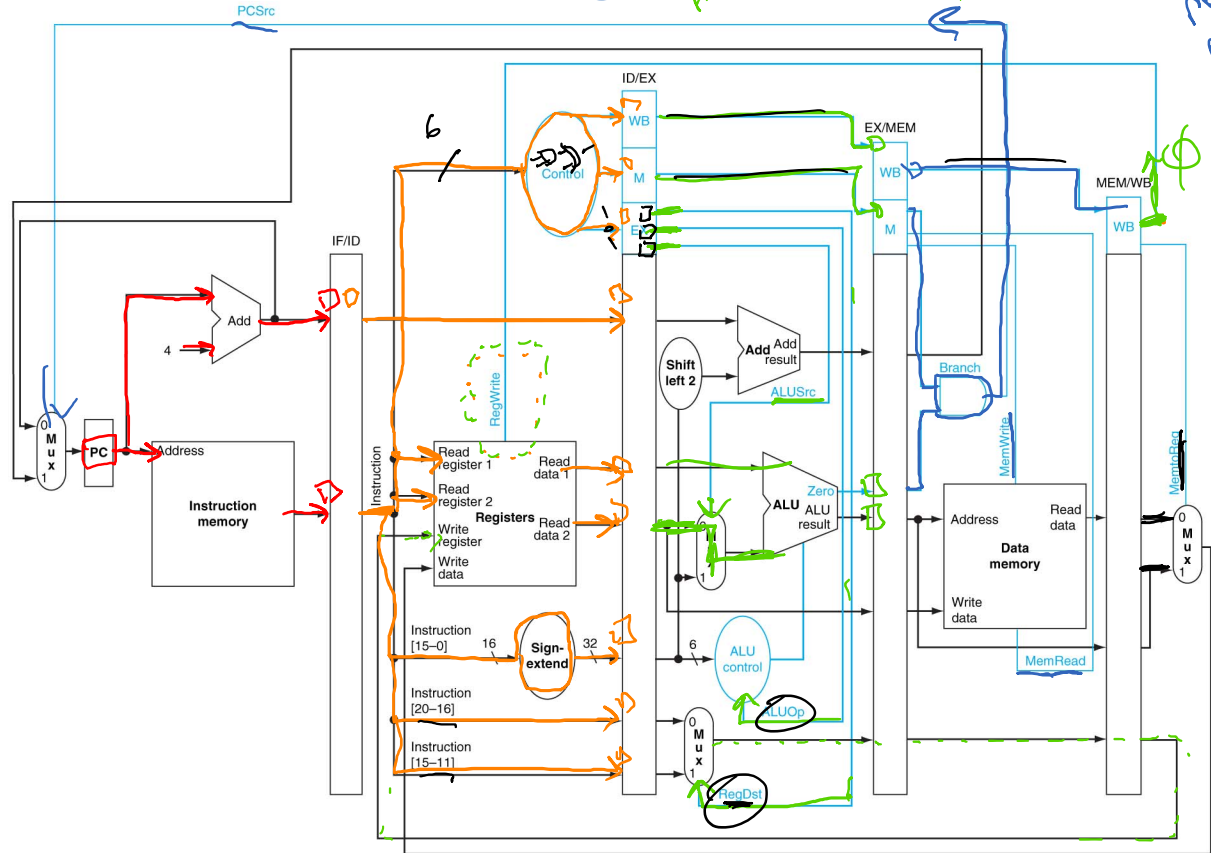

Cycle 5  
RegWr =  $\phi$   
MemW = X

# Is it really that easy?

- What happens when...
  - add \$3, \$10, \$11
  - lw \$8, 1000(\$3)
  - sub \$11, \$8, \$7