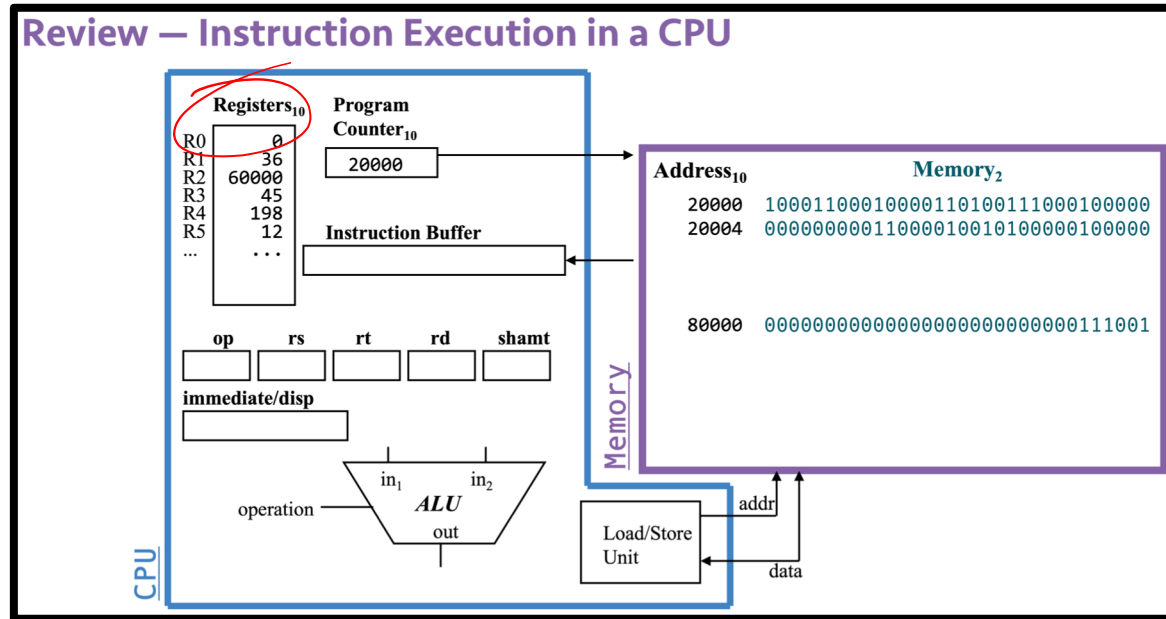


Our previous view of a computer had no organization


- From Part I...




Think about how a MIPS machine executes instructions...

Which correctly describes the *order* things must happen in?

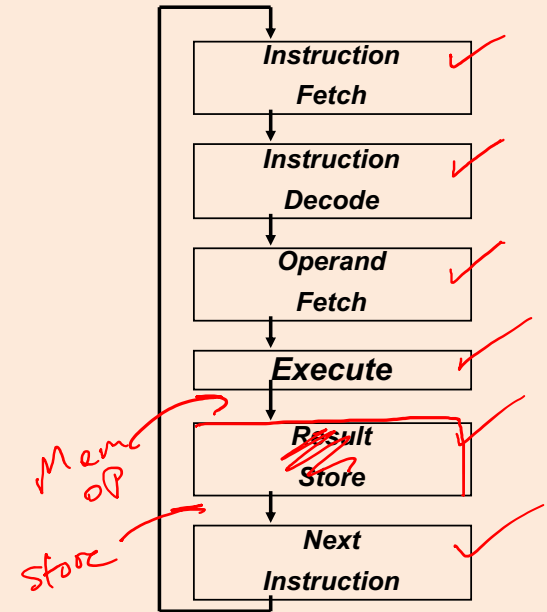- 25 A. The ALU always performs an operation before accessing data memory
- 10 B. The ALU *sometimes* performs an operation before accessing data memory
- 25 C. Data memory is always accessed ~~before~~ *after* performing an ALU operation
- 30 D. Data memory is *sometimes* accessed before performing an ALU operation
- 10 E. None of the above.





 So what does this tell us about what the machine might look like?



Storage Element: Register

  
- Review: D Flip Flop
- New: Register
 - Similar to the D Flip Flop except
 - N-bit input and output
 - Write Enable input
 - Write Enable:
 - 0: Data Out will not change
 - 1: Data Out will become Data In (on the clock edge)



**A register file is a structure that holds many registers.
What kinds of signals will we need for our MIPS register file?**

	Number of bits for register output	Number of bits for register selection	Control Inputs?	Control Outputs?
A	5	32	clk	read/write
B	5	5	clk, read/write	clk
50918 C	32	5	clk, read/write	(none)
D	32	32	clk, read/write	clk, read/write
E	32	5	read/write	(none)

Let's try to make a Register File

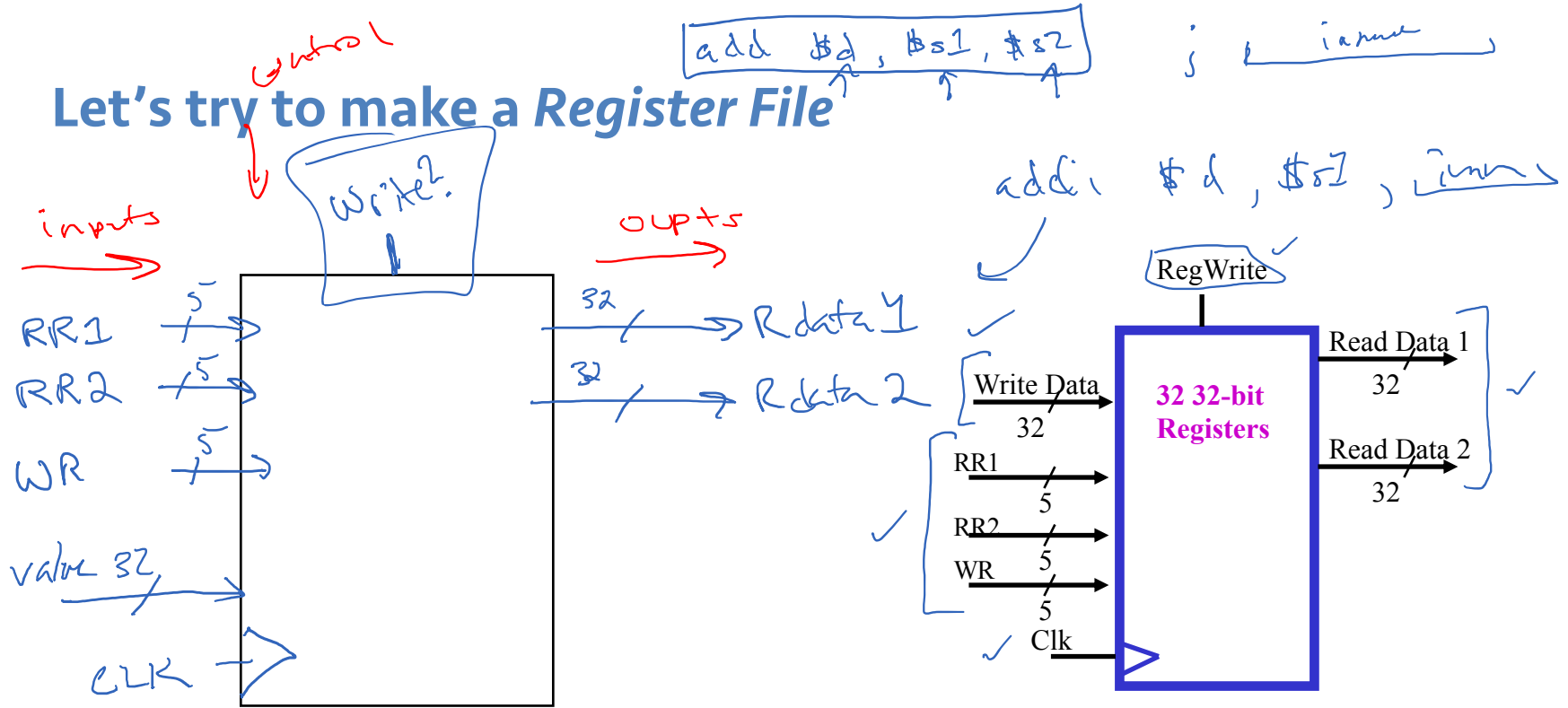

Which of these describes our memory interface (for now)?

30

30



50

A	One 32-bit output	One 5-bit input	One 32-bit input	Clk input	Two 1-bit control inputs
B	One 32-bit output	Two 5-bit inputs		Clk input	Two 1-bit control inputs
C	One 32-bit output		Two 32-bit inputs	Clk input	Two 1-bit control inputs
D	One 32-bit output		One 32-bit input	Clk input	Two 1-bit control inputs
E	<i>None of these are correct</i>				

inputs: address (32-bit)
value (32-bit)

Let's describe the signals to interface to *Memory*

Simple

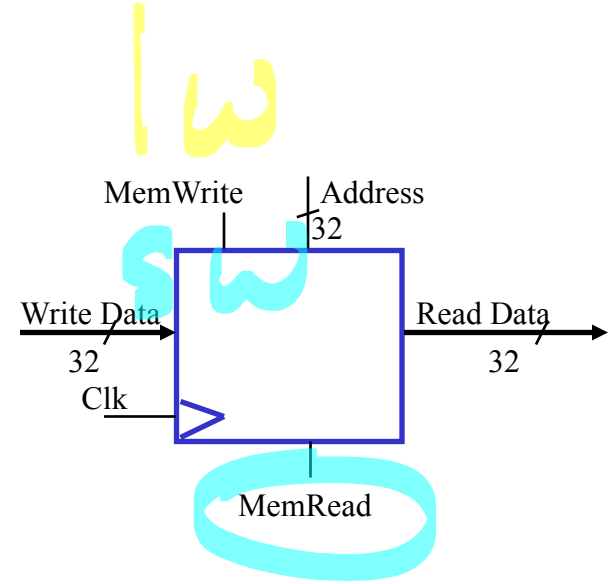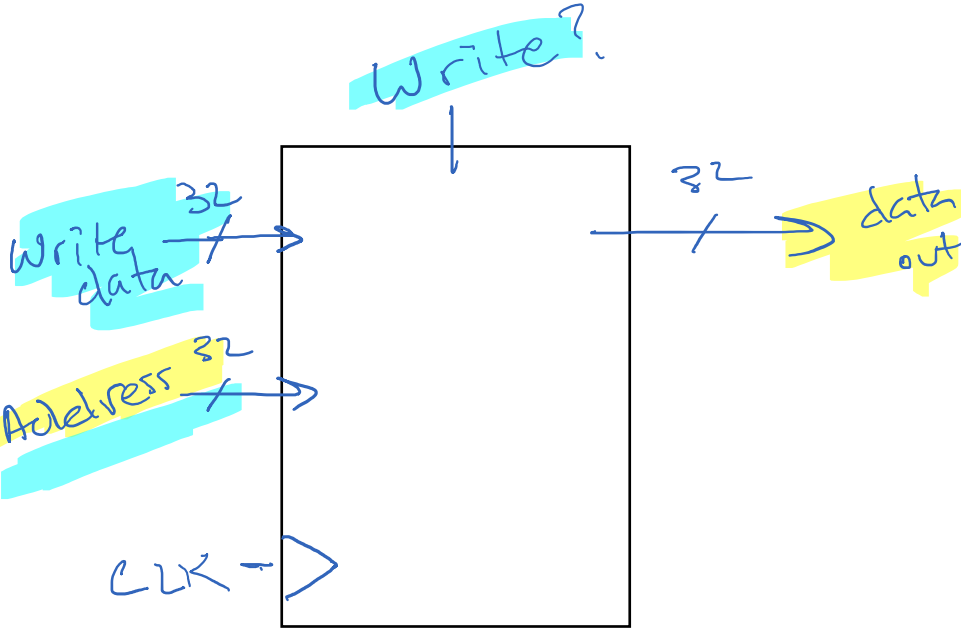


~~eventually~~ eventually: will want Fw (Read?)

Can we layout a high-level design to do everything?

We're ready to look at a simplified MIPS with only:


- memory-reference instructions: `lw`, `sw`
- arithmetic-logical instructions: `add`, `sub`, `and`, `or`, `slt`
- control flow instructions: `beq`

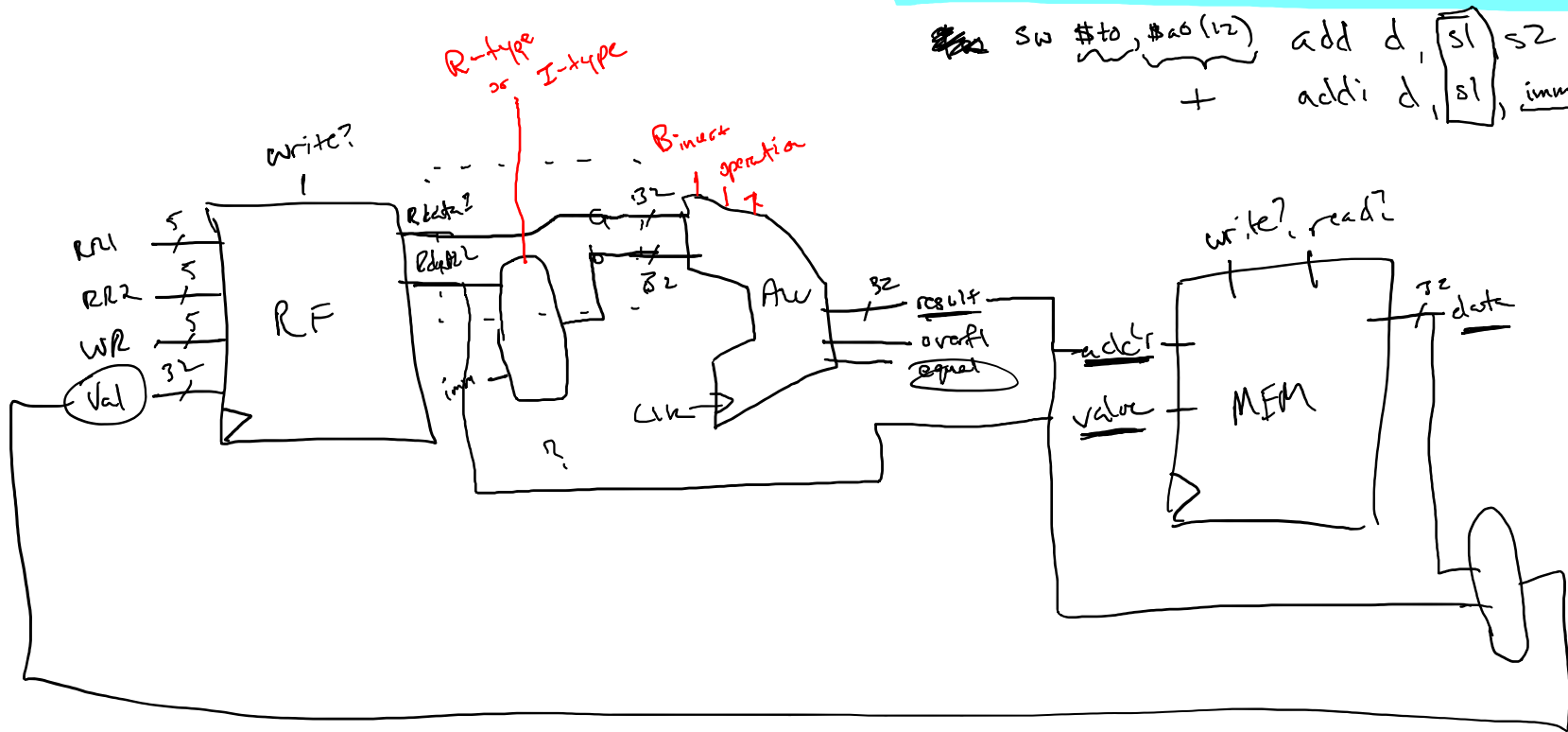~~sw~~ `sw $to, #20($2)` `add d, $s1, $s2`
 + `addi d, $s1, imm`



Putting it All Together: A Single Cycle Datapath

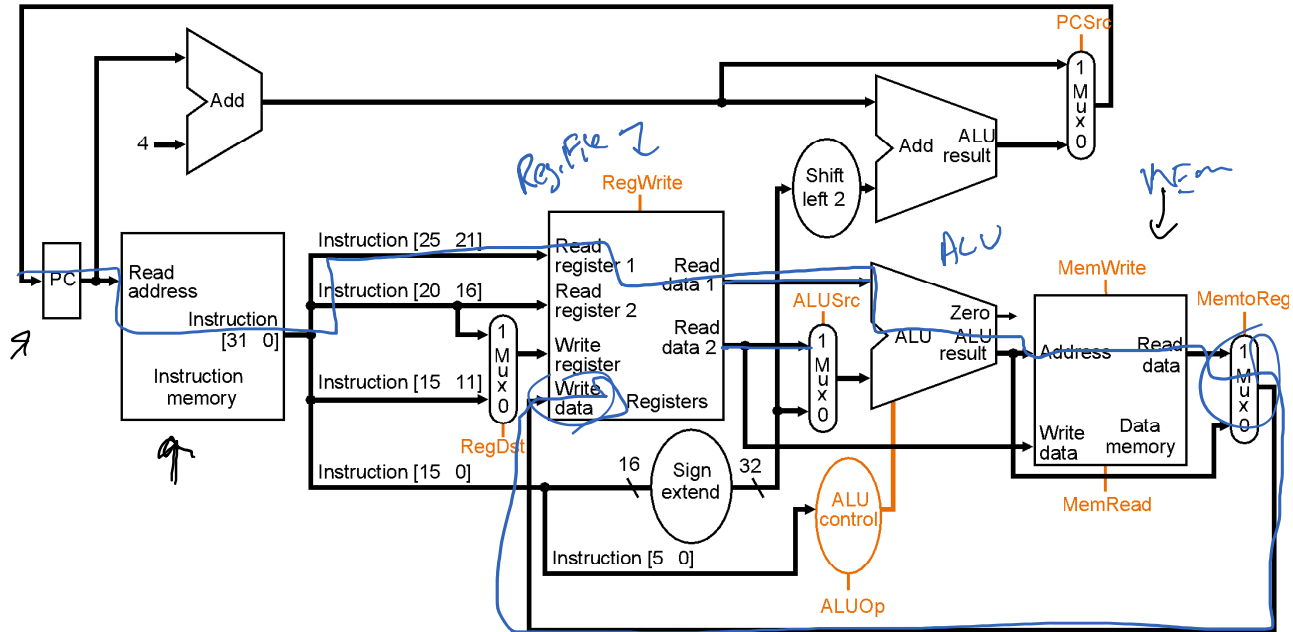
- We have everything except control signals (later)



Active Single-Cycle Datapath

Ignoring control –
which instruction
does this active
datapath represent

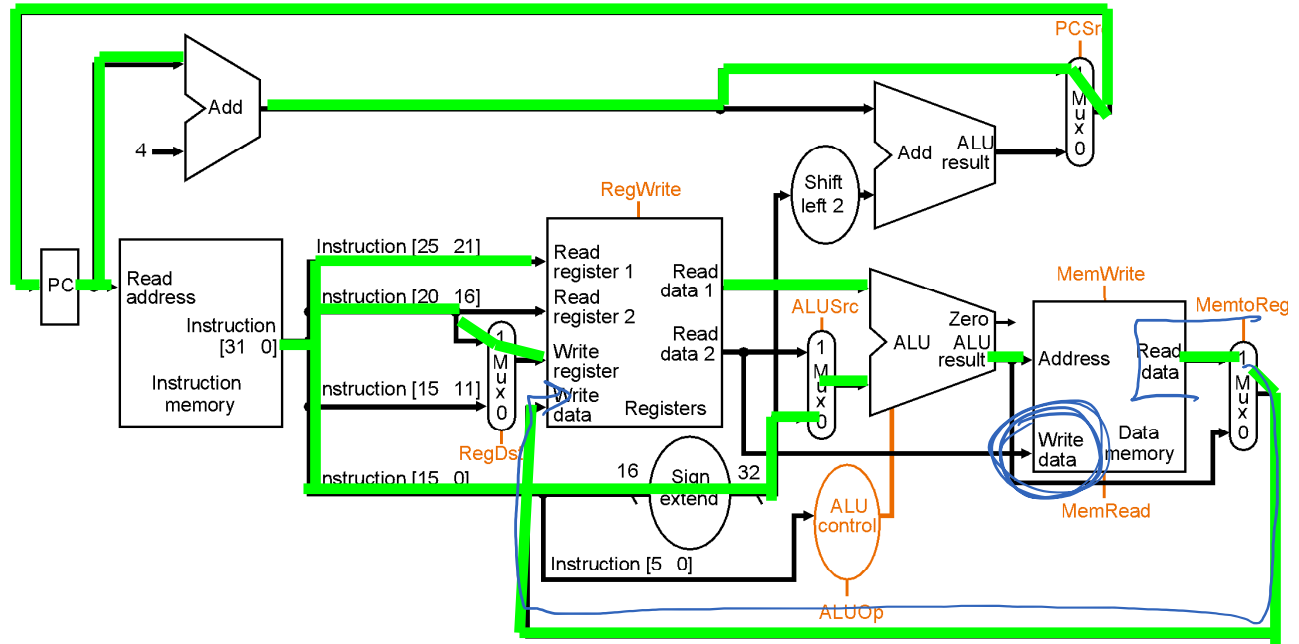
- A. R-type
- B. lw**
- C. sw
- D. Beq
- E. None of the above



Active Single-Cycle Datapath

Ignoring control -
which instruction
does this active
datapath represent

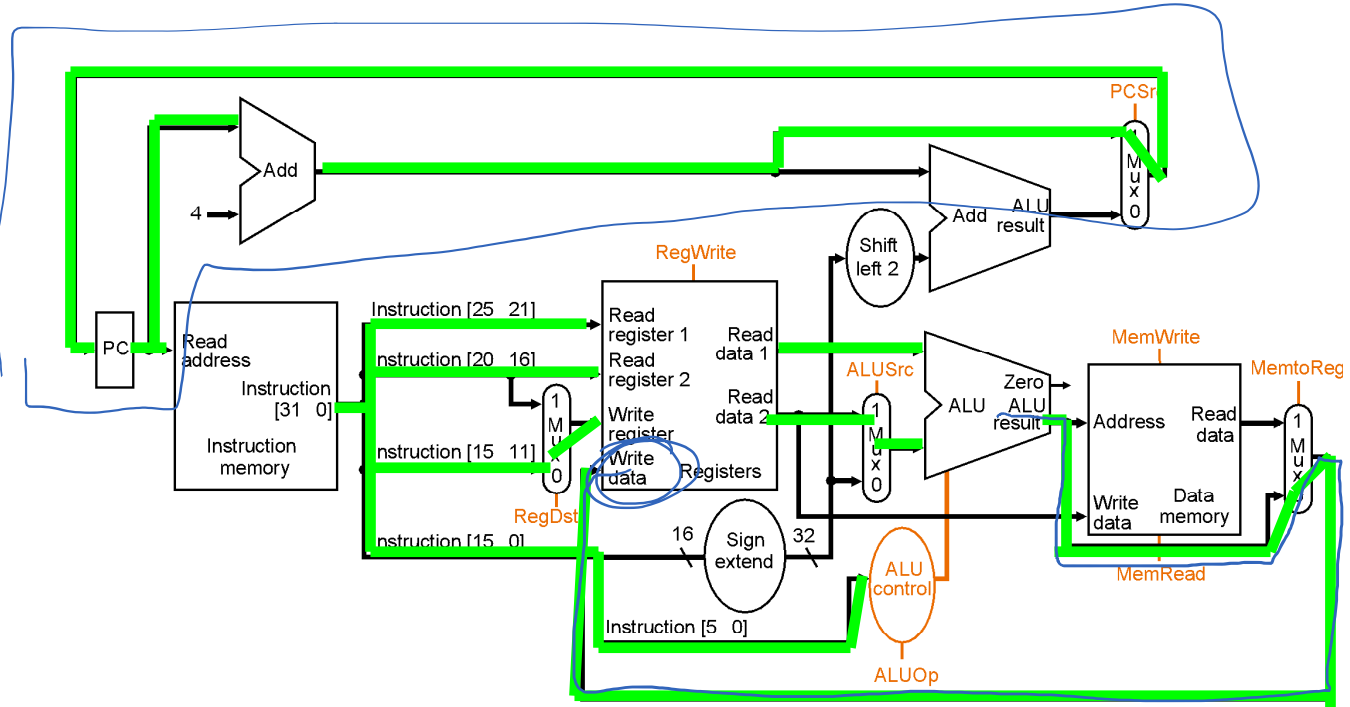
- A. R-type
- B. ~~lw~~
- C. ~~sw~~
- D. ~~Beq~~
- E. None of the above



Active Single-Cycle Datapath

Ignoring control –
which instruction
does this active
datapath represent

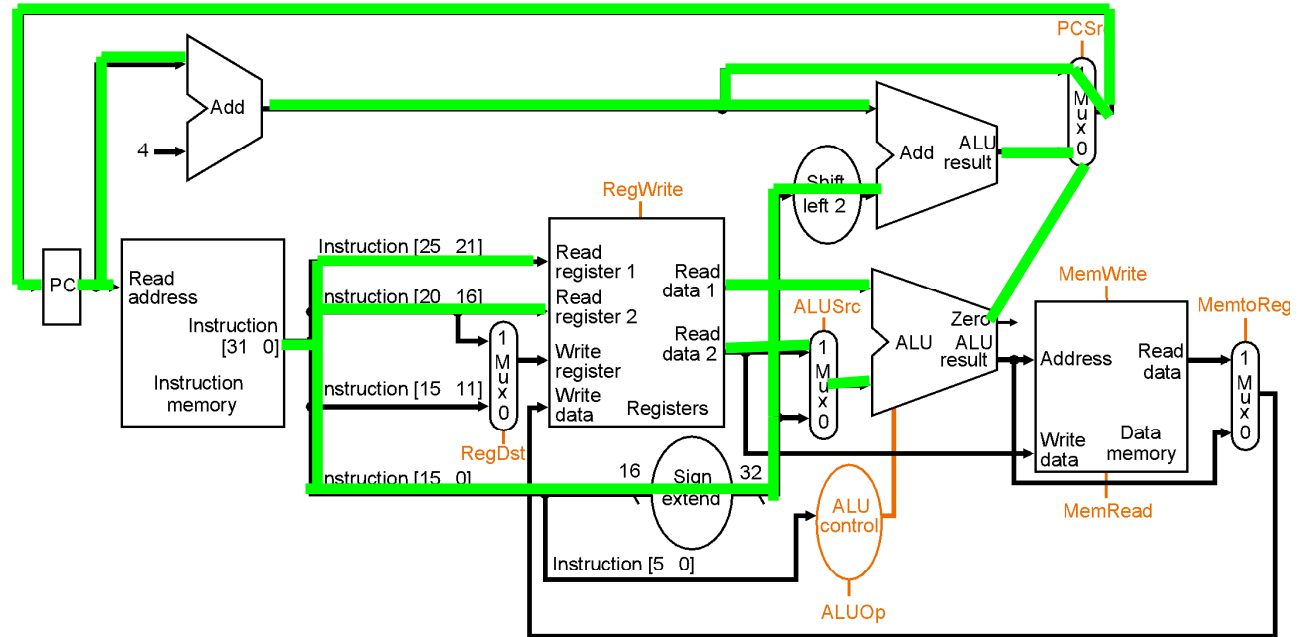
- A. R-type
- B. lw
- C. sw
- D. Beq
- E. None of the above



Active Single-Cycle Datapath

Ignoring control –
which instruction
does this active
datapath represent

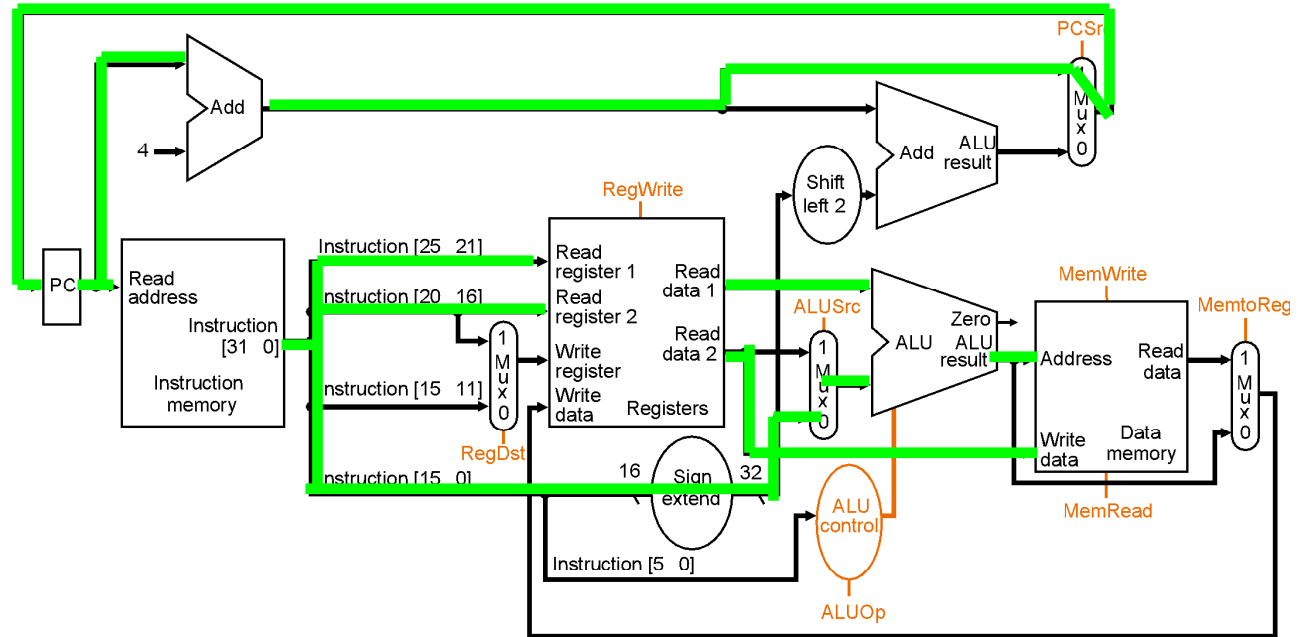- A. R-type
- B. lw
- C. sw
- D. Beq
- E. None of the above



Key Points

- CPU is just a collection of state and combinational logic
- We just designed a very rich processor, at least in terms of functionality
- $ET = IC * CPI * \text{Cycle Time}$
 - where does the single-cycle machine fit in?

“The Control Path”

aka, what controls which wires are green?

Active Single-Cycle Datapath

Ignoring control – which instruction does this active datapath represent

A. R-type
B. lw
C. sw
D. Beq
E. None of the above

Active Single-Cycle Datapath

Ignoring control – which instruction does this active datapath represent

A. R-type
B. lw
C. sw
D. Beq
E. None of the above

Active Single-Cycle Datapath

Ignoring control – which instruction does this active datapath represent

A. R-type
B. lw
C. sw
D. Beq
E. None of the above

Active Single-Cycle Datapath

Ignoring control – which instruction does this active datapath represent

A. R-type
B. lw
C. sw
D. Beq
E. None of the above