

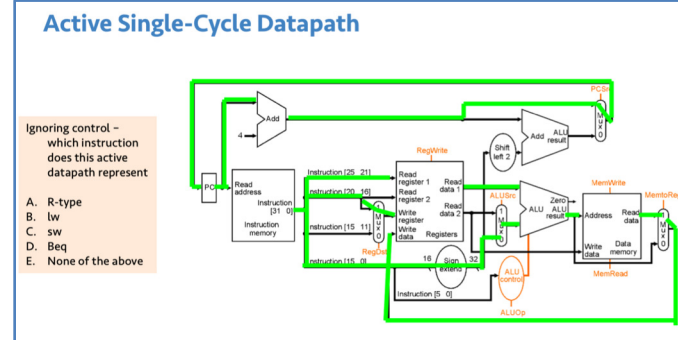
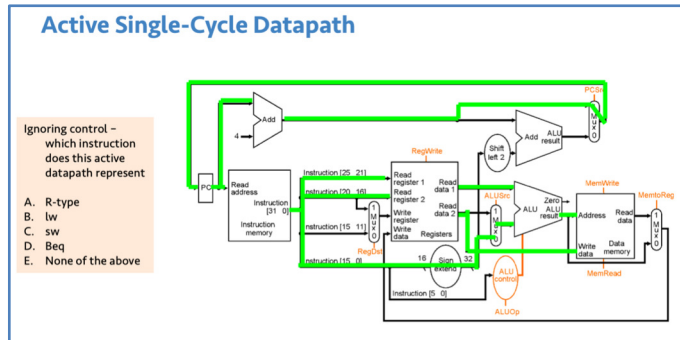
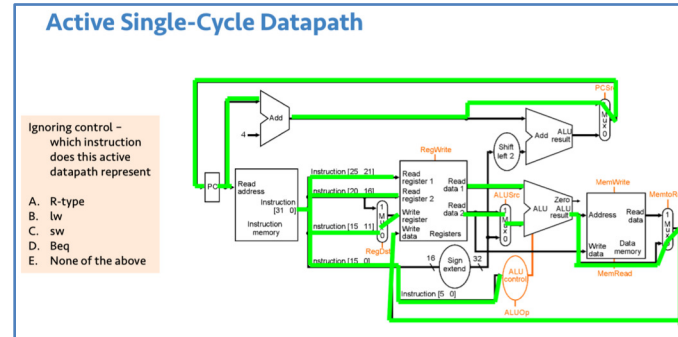


“The Control Path”

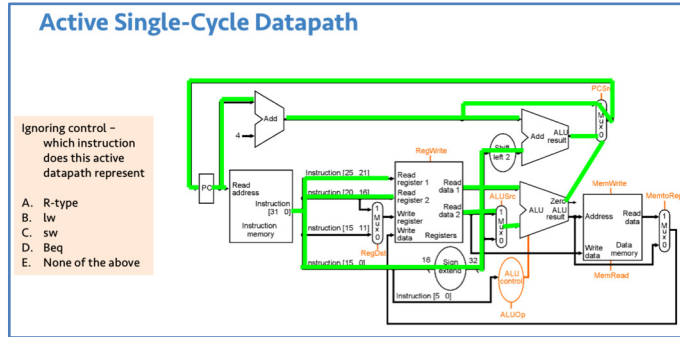aka, what controls which wires are green?




Control signals are all the parts in red



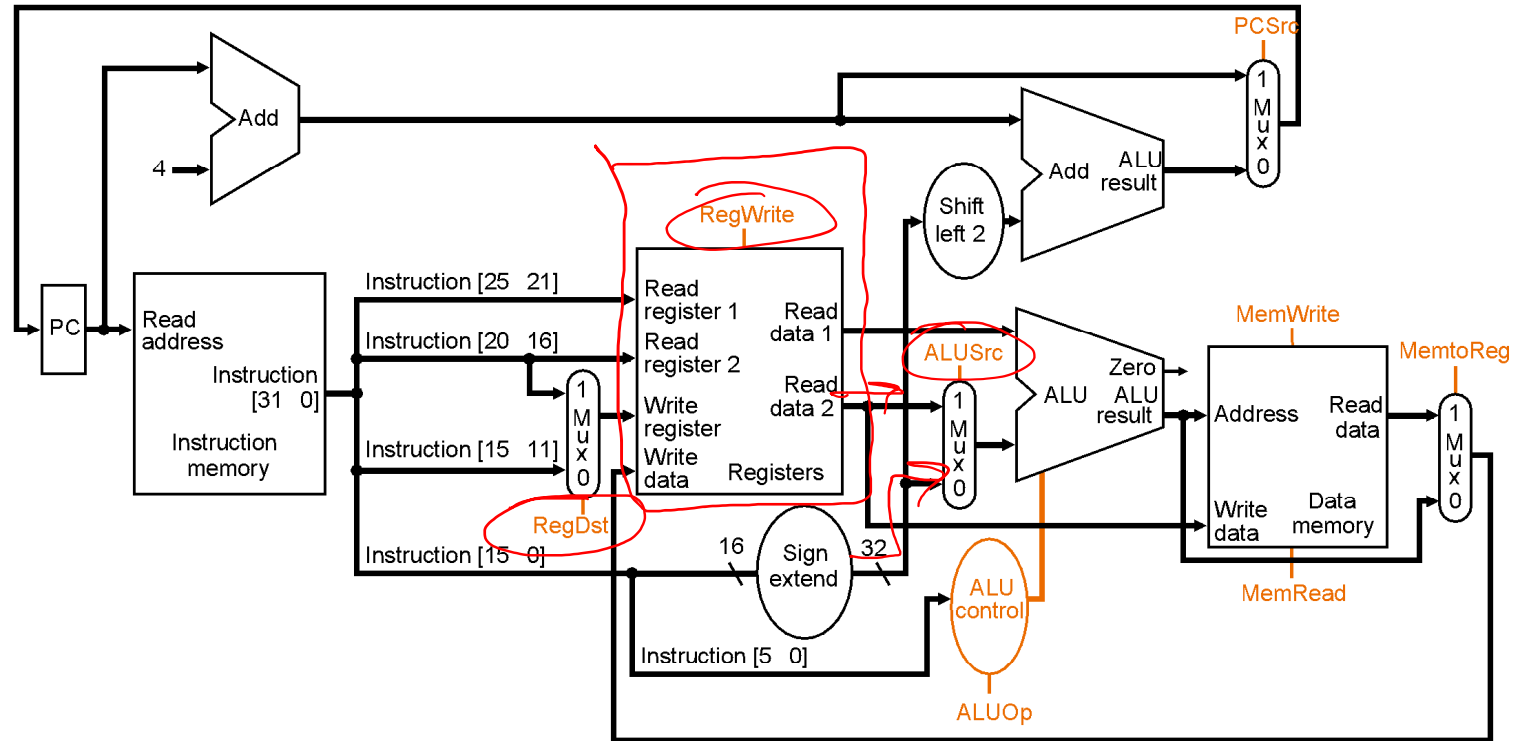


Where might we get control signals?

- Ideas?

Where do we get control signals?

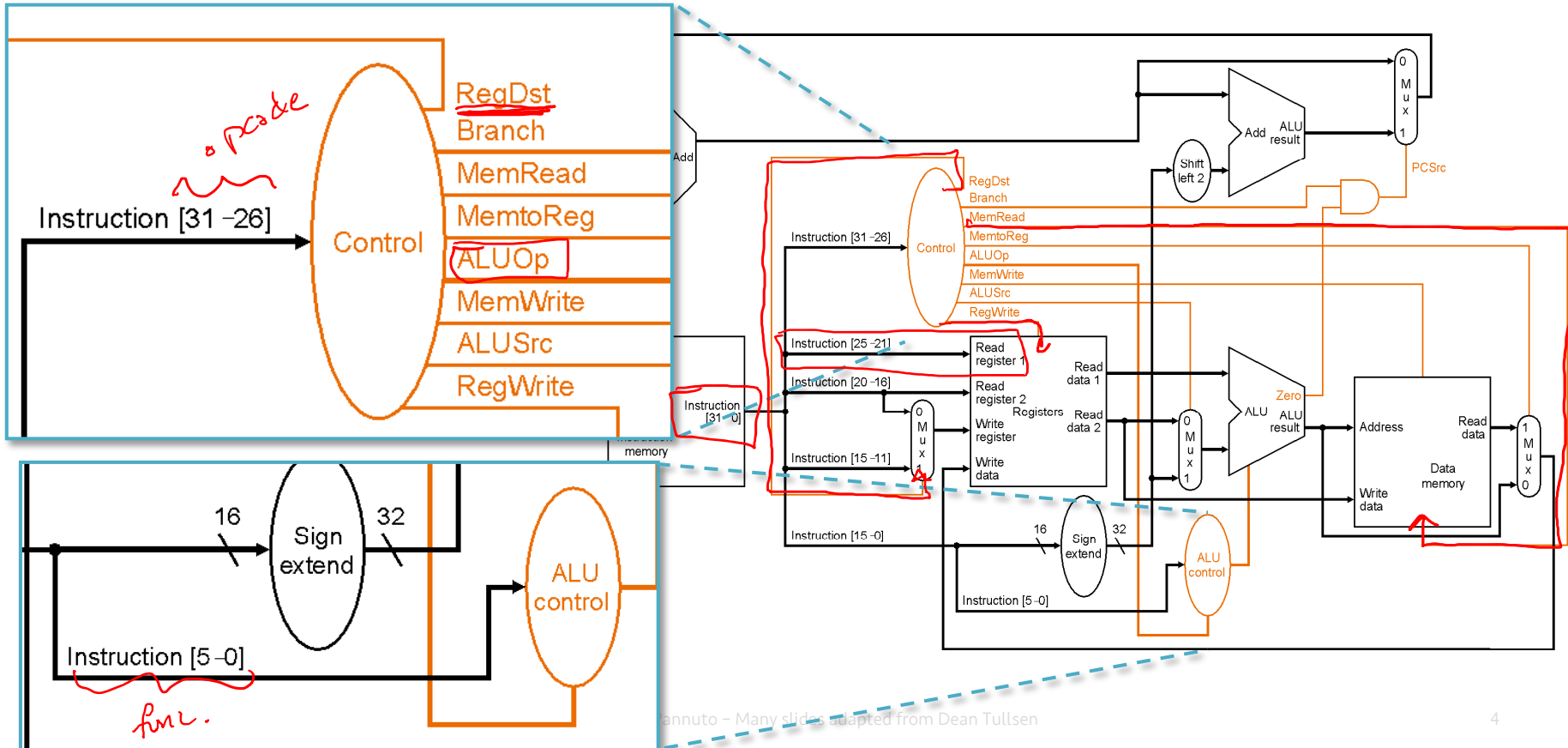

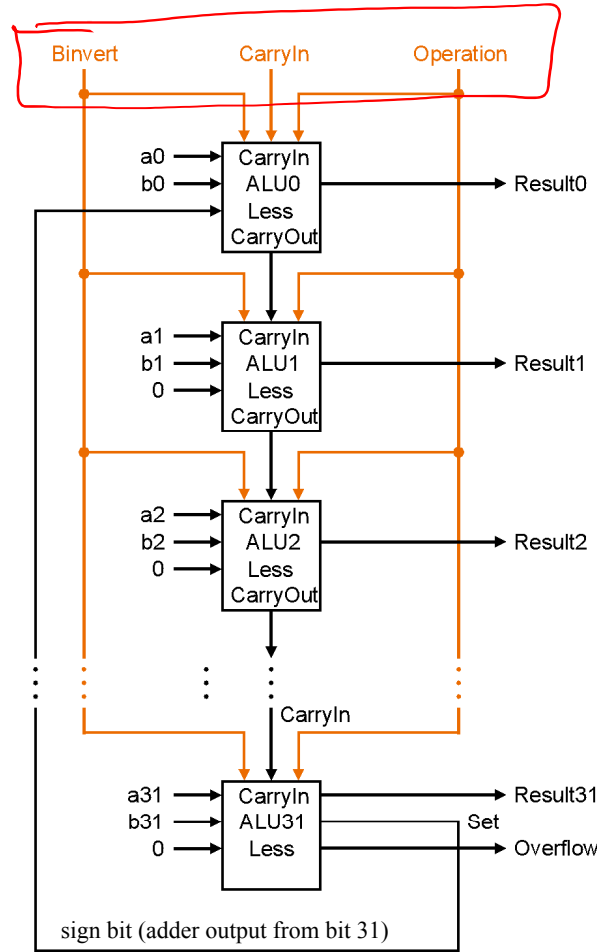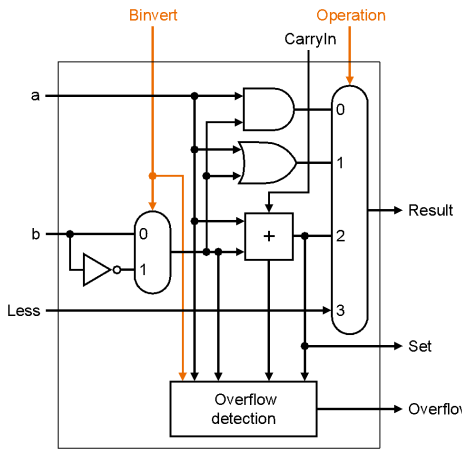 

Recall: The full ALU

| | B _{invert} | Carry _{In} | Operation |
|-----|---------------------|---------------------|-----------|
| and | 0 | x | 0 |
| or | 0 | x | 1 |
| add | 0 | 0 | 2 |
| sub | 1 | 1 | 2 |
| beq | 1 | 1 | 2 |
| slt | 1 | 1 | 3 |

1 - 0-3
2664

3bits ~~ALU~~ ALU

ALU control bits


Note – book presents a 6-function ALU and a fourth ALU control input bit that never gets used (in simplified MIPS machine).

Don't let that confuse you.

- Recall: 5-function ALU


| ALU control input | Function | Operations |
|-------------------|----------|-------------|
| 000 | And | and |
| 001 | Or | or |
| 010 | Add | add, lw, sw |
| 110 | Subtract | sub, beq |
| 111 | Slt | slt |

 - based on **opcode** (bits 31-26) and **function code** (bits 5-0) from instruction
- ALU doesn't need to know all opcodes!
 - Can summarize opcode with ALUOp (2 bits): 00 - lw,sw 01 - beq 10 - R-format



Generating ALU control


| Instruction opcode | ALUOp | Instruction operation | Function code | Desired ALU action | ALU control input |
|--------------------|-------|-----------------------|-------------------|--------------------|-------------------|
| lw | 00 | load word | xxxxxx | add | 010 |
| sw | 00 | store word | xxxxxx | add | 010 |
| beq | 01 | branch eq | xxxxxx | subtract | 110 |
| R-type | 10 | add | 100000 | add | 010 |
| R-type | 10 | subtract | 100010 | subtract | 110 |
| R-type | 10 | AND | 100100 | and | 000 |
| R-type | 10 | OR | 100101 | or | 001 |
| R-type | 10 | slt | 101010 | slt | 111 |

 

Generating individual ALU signals

| ALUop | Function | ALUctr signals |
|-------|----------|----------------|
| 00 | xxxx | 010 |
| 01 | xxxx | 110 |
| 10 | 0000 | 010 |
| 10 | 0010 | 110 |
| 10 | 0100 | 000 |
| 10 | 0101 | 001 |
| 10 | 1010 | 111 |

opcode *func*

 


$$\text{ALUctr2} = (!\text{ALUop1} \ \& \ \text{ALUop0}) \ | \ (\text{ALUop1} \ \& \ \text{Func1})$$

$$\text{ALUctr1} = \text{ALUop1} \ \& \ !\text{Func2} \ | \ (\text{ALUop1} \ \& \ !\text{Func2})$$

$$\text{ALUctr0} = \text{ALUop1} \ \& \ (\text{Func0} \ | \ \text{Func3})$$

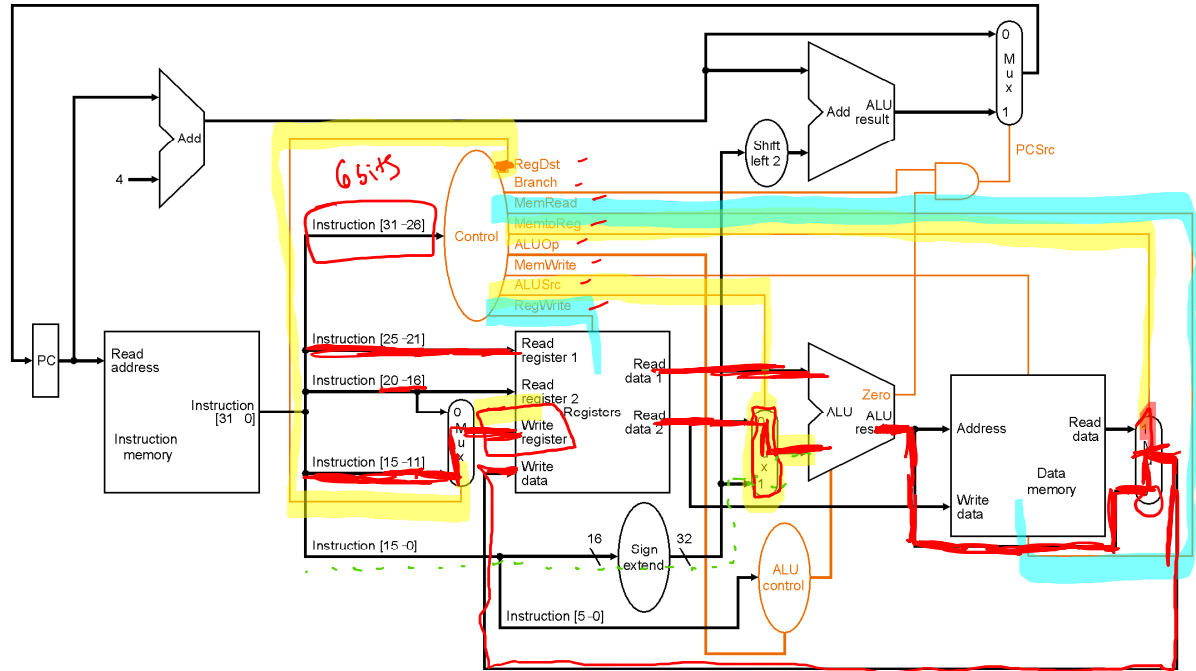R-Format Instructions (e.g., add \$d, \$s0, \$s1)




| Instruction | RegDst | ALUSrc | Memto-Reg | Reg Write | Mem Read | Mem Write | Branch | ALUOp1 | ALUOp0 |
|-------------|--------|--------|-----------|-----------|----------|-----------|--------|--------|--------|
| R-format | 1 | 0 | 0 | 1 | 0 | 0 | 0 | 1 | 0 |
| lw | | | | | | | | 0 | 0 |
| sw | | | | | | | | 0 | 0 |
| beq | | | | | | | | 0 | 1 |

op code r r r
op code r r imm


lw instruction control signals?

| | ALUSrc | RegDst | MemtoReg |
|---|-------------------|--------|----------|
| A | 0 | 0 | 0 |
| B | 1 | X | 0 |
| C | 1 | 0 | 1 |
| D | 1 | 1 | 1 |
| E | None of the above | | |

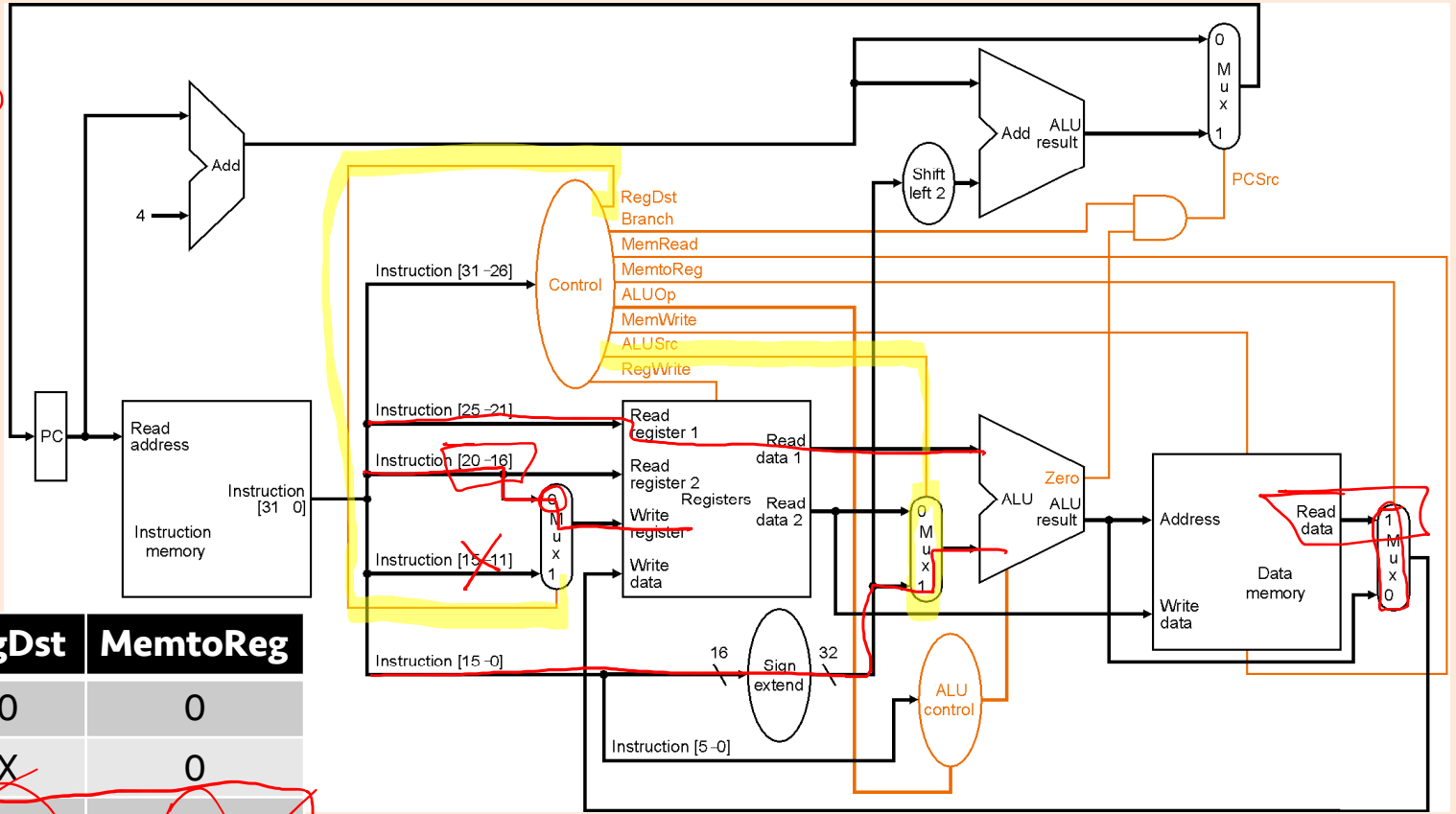

lw-type lw \$d, \$s(10) - addr
↑ ↑ ↑
r s imm


lw Control

 


| Instruction | RegDst | ALUSrc | Memto-Reg | Reg Write | Mem Read | Mem Write | Branch | ALUOp1 | ALUp0 |
|-------------|--------|--------|-----------|-----------|----------|-----------|--------|--------|-------|
| R-format | 1 | 0 | 0 | 1 | 0 | 0 | 0 | 1 | 0 |
| lw | | | | | | | | 0 | 0 |
| sw | | | | | | | | 0 | 0 |
| beq | | | | | | | | 0 | 1 |

sw instruction control signals?


| | ALUSrc | RegDst | MemtoReg |
|---|-------------------|--------|----------|
| A | 0 | 0 | 0 |
| B | 1 | X | 0 |
| C | 0 | 0 | X |
| D | 1 | X | 1 |
| E | None of the above | | |

 

sw Control

 [illegible]



beq Control

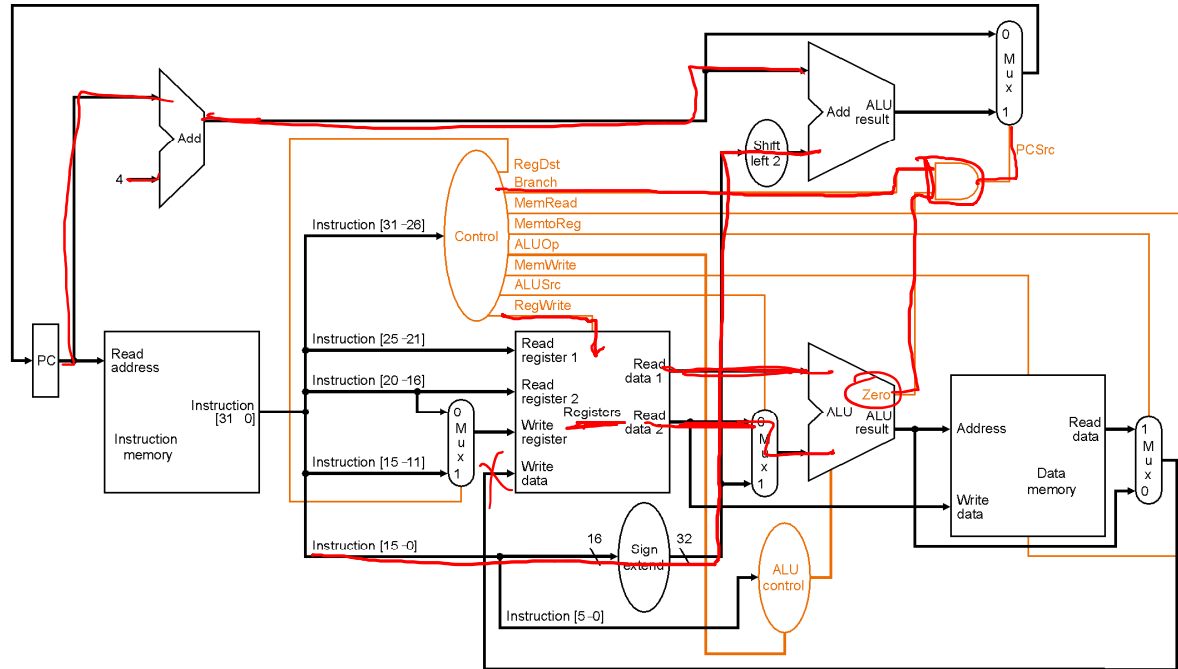

| Instruction | RegDst | ALUSrc | Memto-Reg | Reg Write | Mem Read | Mem Write | Branch | ALUOp1 | ALUp0 |
|-------------|--------|--------|-----------|-----------|----------|-----------|--------|--------|-------|
| R-format | 1 | 0 | 0 | 1 | 0 | 0 | 0 | 1 | 0 |
| lw | 0 | 1 | 1 | 1 | 1 | 0 | 0 | 0 | 0 |
| sw | X | 1 | X | 0 | 0 | 1 | 0 | 0 | 0 |
| beq | X | 0 | X | 0 | 0 | 0 | 1 | 0 | 1 |


Control Truth Table

| | | R-format | lw | sw | beq |
|---------------|----------|-----------------|-----------|-----------|------------|
| Opcode | | 000000 | 100011 | 101011 | 000100 |
| Outputs | RegDst | 1 | 0 | x | x |
| | ALUSrc | 0 | 1 | 1 | 0 |
| | MemtoReg | 0 | 1 | x | x |
| | RegWrite | 1 | 1 | 0 | 0 |
| | MemRead | 0 | 1 | 0 | 0 |
| | MemWrite | 0 | 0 | 1 | 0 |
| | Branch | 0 | 0 | 0 | 1 |
| | ALUOp1 | 1 | 0 | 0 | 0 |
| | ALUOp0 | 0 | 0 | 0 | 1 |

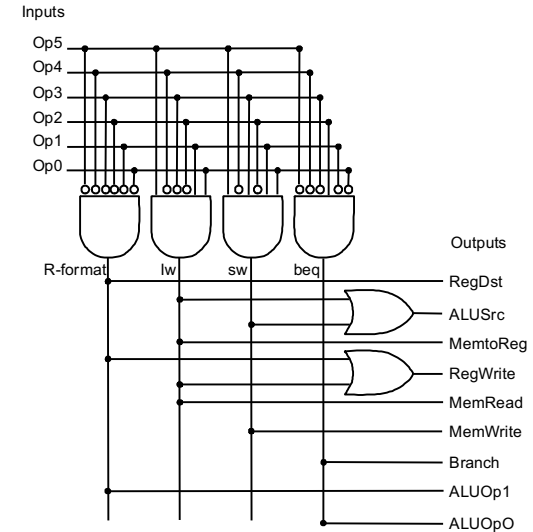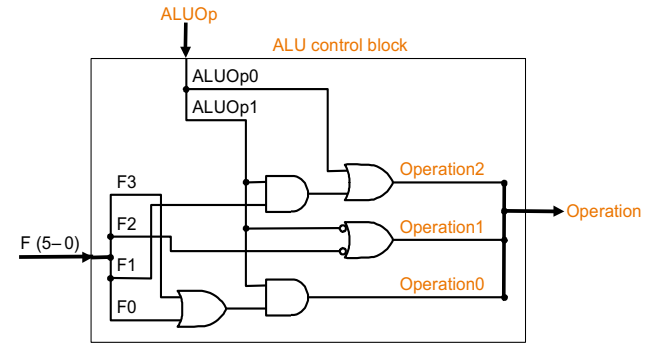


add i

↳ P-type

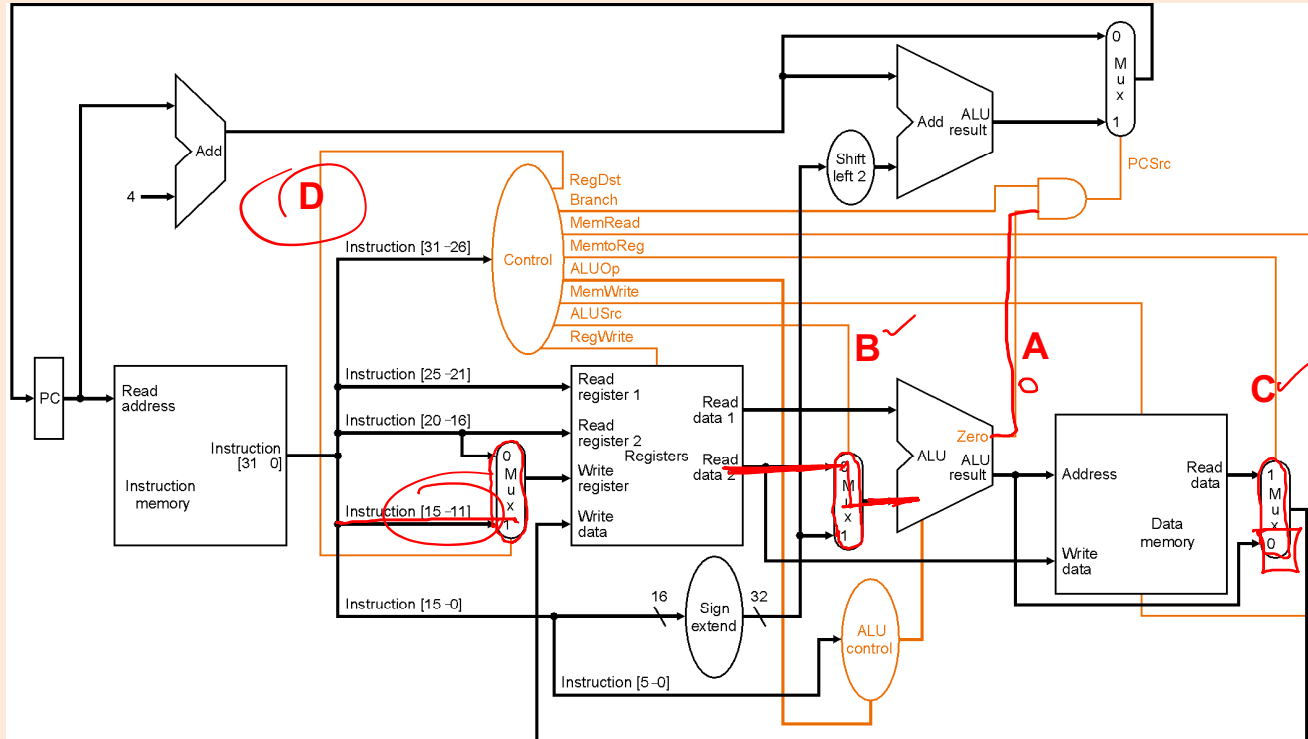

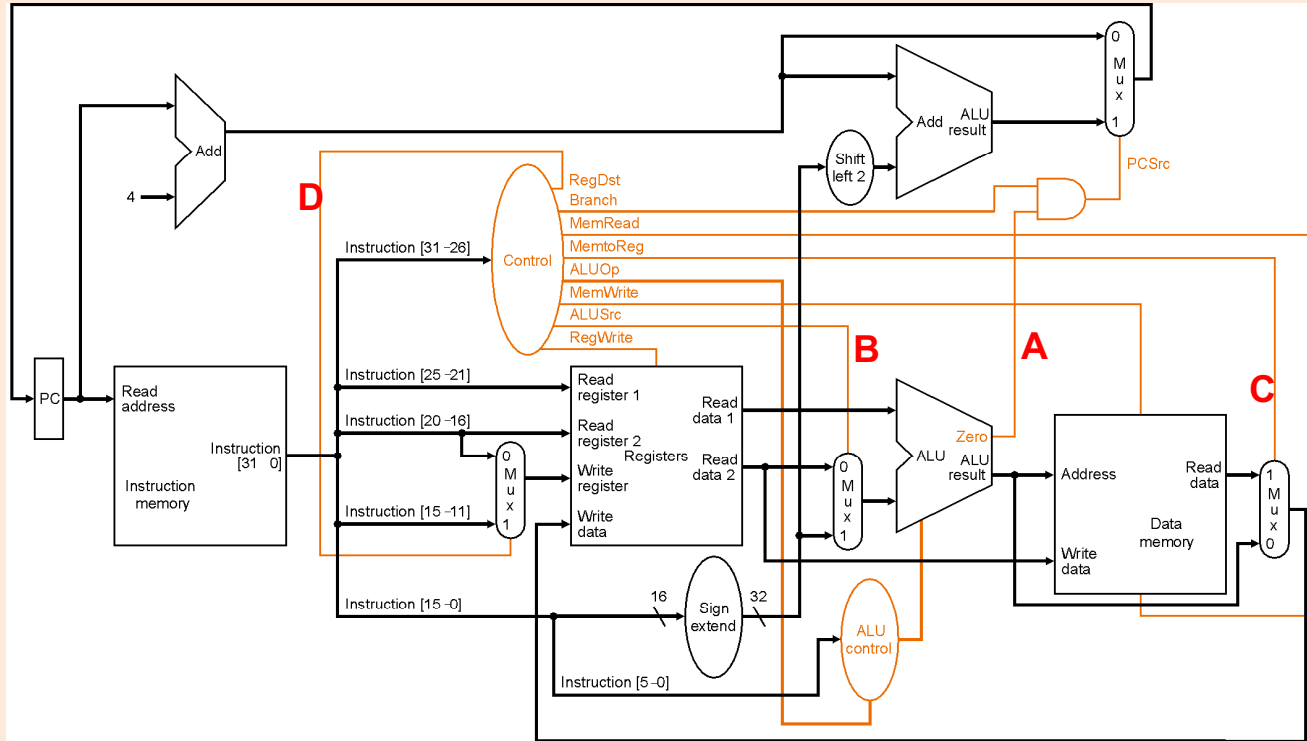Which wire – if always **ONE** – would break **lw**?




~~Single-Cycle~~ CPU Summary

- Easy, particularly the control
- Which instruction takes the longest?
 - By how much? Why is that a problem?
- $ET = IC * CPI * CT$
- What else can we do?
- When does a **multi-cycle implementation** make sense?
 - e.g., 70% of instructions take 75 ns, 30% take 200 ns?
 - suppose 20% overhead for extra latches
- Real machines have much **more** variable instruction latencies than this.

Let's think about this multicycle processor...


- (a very brief introduction...)

Why a Multiple Clock Cycle CPU?

 



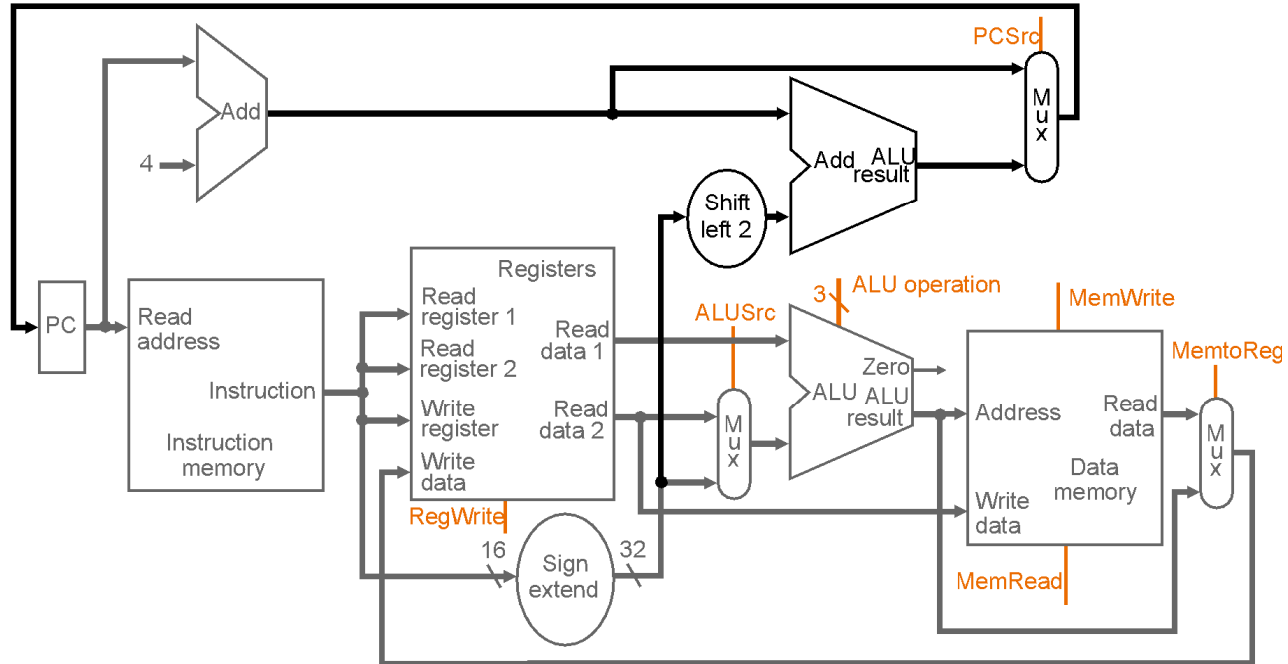

- the problem => single-cycle cpu has a cycle time long enough to complete the longest instruction in the machine
- the solution => break up instruction execution into smaller tasks, each task taking one cycle
 - different instructions require different numbers of tasks (of cycles)
- other advantages => reuse of functional units (e.g., alu, memory)

High-level View



So Then,

- How many cycles does it take to execute
 - Add 
 - BNE 
 - LW 
 - SW 
- What about control logic?
- $ET = IC * CPI * CT$



Summary of instruction execution steps

"step" == "task" == " _____ "

4

5

3

| Step | R-type | Memory | Branch |
|---|---|--|---|
| Instruction Fetch ✓ | $IR = Mem[PC]$ $PC = PC + 4$ | | |
| Instruction Decode/ register fetch ✓ | $A = Reg[IR[25-21]]$ $B = Reg[IR[20-16]]$ $ALUout = PC + (sign-extend(IR[15-0]) \ll 2)$ | | |
| Execution, address computation, branch completion ✓ | $ALUout = A \text{ op } B$ | $ALUout = A +$ sign- extend($IR[15-0]$) | if ($A==B$) then $PC=ALUout$ |
| Memory access or R- type completion ✓ | $Reg[IR[15-11]] =$ $ALUout$ | memory-data = $Mem[ALUout]$ or $Mem[ALUout] =$ B |  |
| Write-back | | $Reg[IR[20-16]] =$ memory-data |  |

What is the fastest, slowest class of instruction in this MC machine?

Multicycle Questions

- How many cycles will it take to execute this code?

```
lw    $t2, 0($t3)
lw    $t3, 4($t3)
beq   $t2, $t3, Label    #assume not taken
add   $t5, $t2, $t3
sw    $t5, 8($t3)
Label: ...
```

| How many cycles to execute these 5 instructions? | |
|--|-------------------|
| A | 5 |
| B | 25 |
| C | 22 |
| D | 21 |
| E | None of the above |

Multicycle Implications

```
lw    $t2, 0($t3)
lw    $t3, 4($t3)
#assume not taken
beq   $t2, $t3, Label1
add   $t5, $t2, $t3
sw    $t5, 8($t3)
Label: ...
```

- What is the CPI of this program?
- What about a program that is 20% loads, 10% stores, 50% R-type, and 20% branches?

Single-Cycle, Multicycle CPU Summary

- Single-cycle CPU
 - CPI = 1, CT = LONG, simple design, simple control
 - No one has built a single-cycle machine in many decades
- Multi-cycle CPU
 - CPI > 1, CT = fairly short, complex control
 - Common up until maybe early 1990s, and dominant for many decades before that.

$$ET = CPI^{\uparrow} * CT^{\downarrow\downarrow}$$